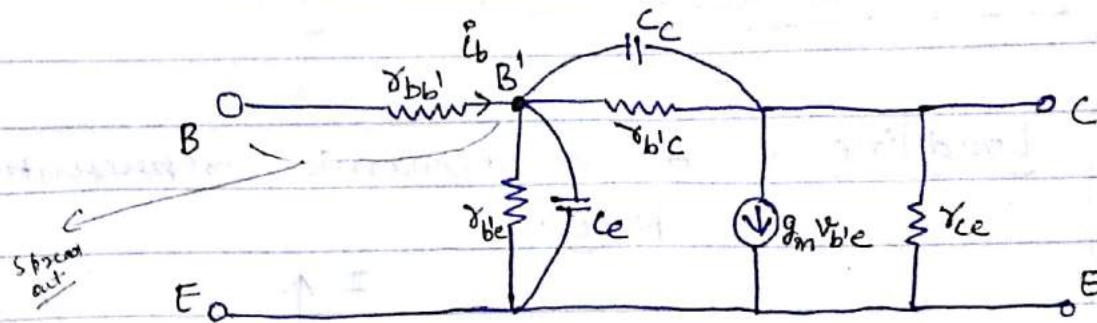


[High frequency analysis of BJT] :-

This model proposed by Giga Colletto —





Due to high frequency, Now circuit will become reactive.

* All external capacitance are short circuited and all internal capacitance are open circuited.

↑ γ is scattered value m + k/f

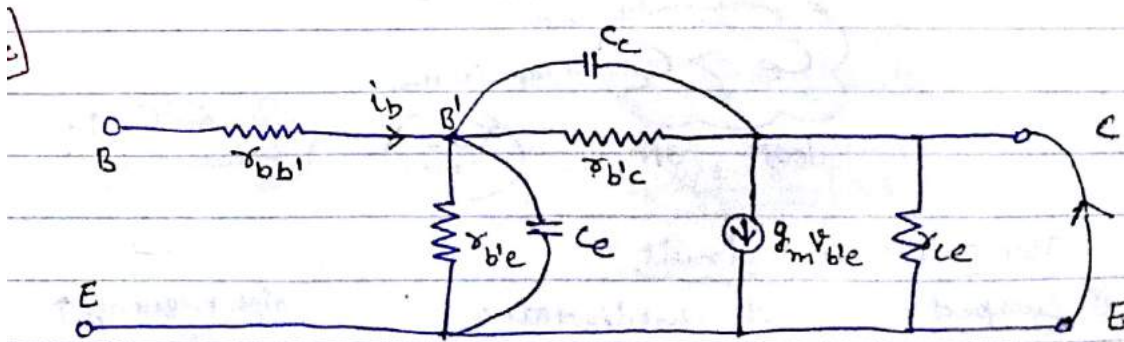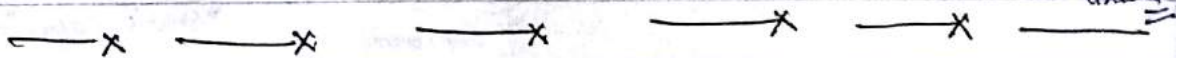
↓ value in pF so we treat as open circuit




$$g_m = \frac{i_c}{v_{b'e}} \bigg|_{V_{CE}=0}$$

$g_m \rightarrow$ Short circuit trans conductance gain

$$g_m = \frac{\partial i_c}{\partial v_{B'E}} \bigg|_{V_{CE}=0}$$

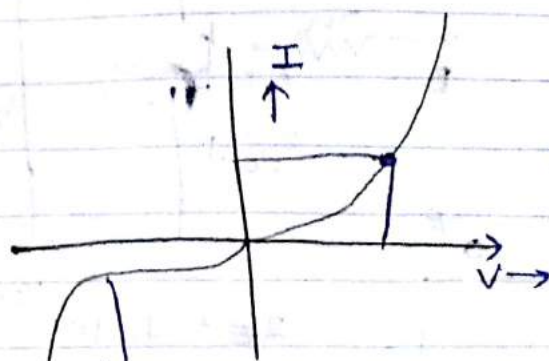

$I_Q \rightarrow$ Quiescent current

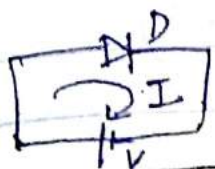

$$I = I_0 (e^{V/V_T} - 1)$$

$$V_T = \frac{kT}{q} ; 26\text{mV at } 29^\circ\text{C}$$

$I_0 \rightarrow$ It doubles for every increase in 10°C .

Diode equation

$V_T \rightarrow$ Thermal voltage

$I_0 \rightarrow$ Reverse saturation current



Forward: $I = I_0 e^{V/V_T}$

Reverse: $I \approx -I_0$

$$\frac{dI}{dV} = \frac{I_0 e^{V/V_T}}{V_T} \approx \frac{I_Q}{V_T}$$

dynamic resistance

$$r = \frac{V_T}{I_Q}$$

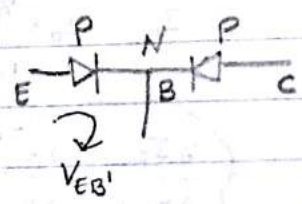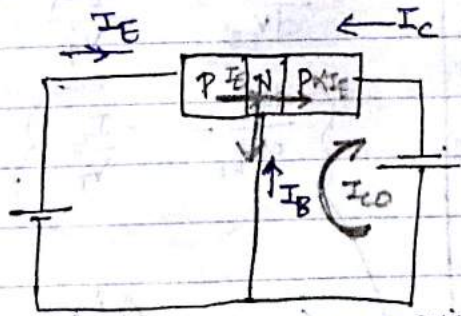


$$I_E = I_C + I_B$$

$$I_C = I_{C0} - \alpha I_E$$

reverse saturation current in base-collector junction

Transistor equation

always +ve either in PNP or NPN

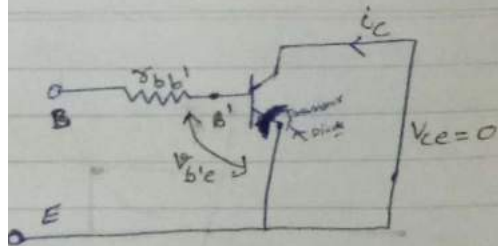

$$I_E = I_0 (e^{V_{EB}/V_T} - 1)$$

$$\frac{dI_E}{dV_{EB}} = \frac{I_0 e^{V_{EB}/V_T}}{V_T} \approx \frac{I_E}{V_T}$$

$$\gamma_E = \frac{V_T}{I_E}$$

$$\frac{dI_C}{dV_{EB}} = I_{C0} - \alpha I_E$$

$$\frac{dI_C}{dV_{EB}} = 0 - \frac{\alpha}{\gamma_E}$$

$$\frac{dI_C}{dV_{EB}} = -\frac{I_E \alpha}{V_T}$$

$$\frac{dI_C}{dV_{BE}} = -\frac{I_C}{V_T}$$

$$i_c = \Delta i_q$$

$$i_q = I_{CQ} + i_c$$

$$\frac{i_c}{V_{be}} = -\frac{I_C}{V_T}$$

$$g_m = -\frac{I_{CQ}}{V_T}$$



Ques- For a NPN transistor the Q-point collector current is 1.3 mA . If the transistor is operated at room temp calculate the short circuit trans conductance gain of such a condensor. If suddenly the Q-point of the transistor is shifted & now the collector current (Q-point) is maintain 10-times of the earlier new what will be Transconductance gain? what do you conclude from these 2 options?

Sol:-

$$i) \quad g_m = \frac{I_{CQ}}{V_T} = \frac{1.3 \text{ mA}}{26 \text{ mV}} \approx 0.05 \text{ S} \approx 50 \text{ mA/V}$$

$$ii) \quad g_m = 0.5 \approx 500 \text{ mA/V}$$

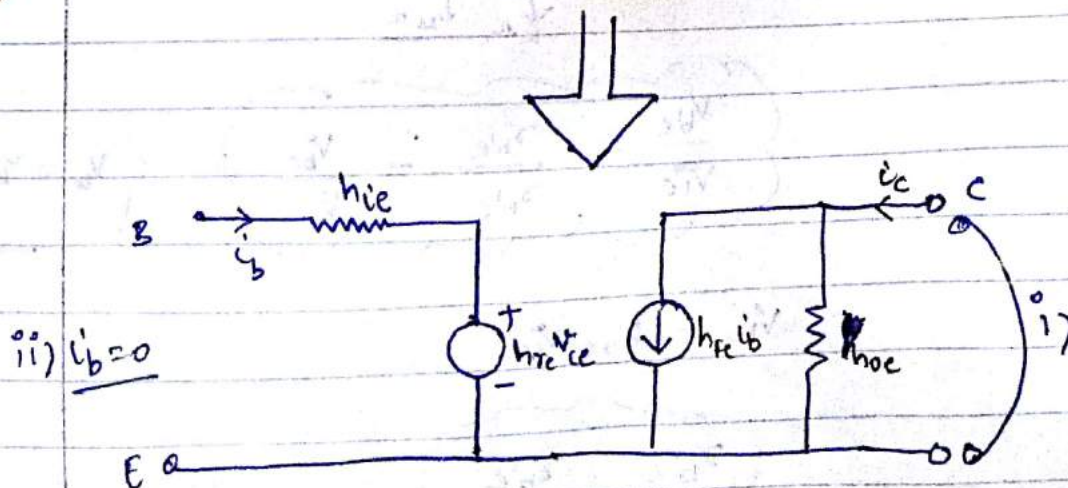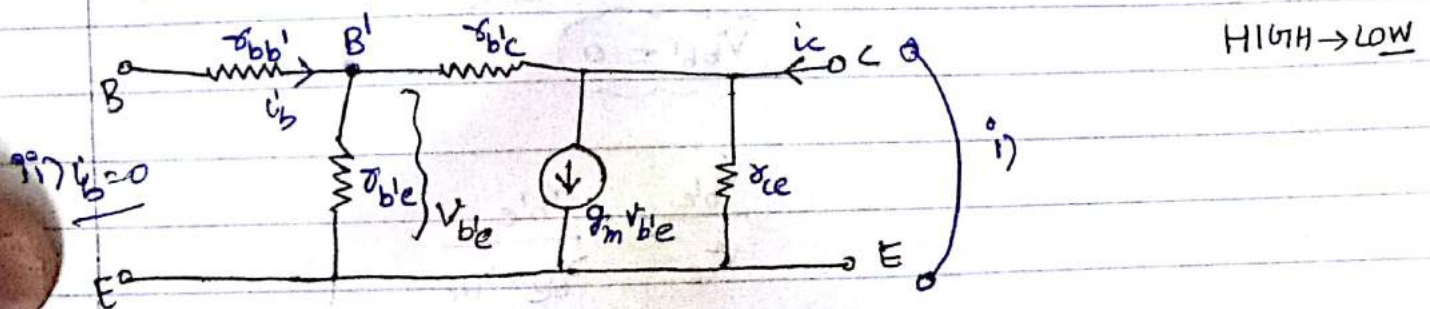BJT Transistor provides us a trans conductance gain of 500 mA/V but FET unable to provide 500 mA/V it only provide us with difficulty 50 mA/V



i) $i_c = h_{fe} i_b$
 $i_c = g_m v_{be}$

or $g_m v_{be} = h_{fe} i_b$

$$\frac{v_{be}}{i_b} = \frac{h_{fe}}{g_m} \bigg|_{v_{ce}=0}$$

Now $r_{b'e} \rightarrow$ base collector small signal dynamic resistance
 $\downarrow M\Omega$ it is very large compare to $r_{b'e}$.

So;

$$r_{b'e} = \frac{v_{be}}{i_b} \bigg|_{v_{ce}=0}$$

ii)

$i_b = 0$ then

$$r_{b'e} = \frac{h_{fe}}{g_m} \approx 1K\Omega$$

$$v_{b'b} = 0$$

$$\frac{v_{be}}{v_{ce}} = \frac{r_{b'e}}{r_{b'e} + r_{b'c}}$$

$\downarrow K\Omega$ $\downarrow M\Omega$

$$\frac{v_{be}}{v_{ce}} = \frac{r_{b'e}}{r_{b'c}} = \frac{v_{be}}{v_{ce}} \quad \left\{ v_{be} = v_{b'e} \right\}$$

$$v_{b'e} = h_{re} v_{ce}$$

$$r_{b'c} = \frac{r_{b'e}}{h_{re}}$$

$$\approx 4M\Omega$$

iii)

$$i_c = V_{ce} g_{ce} + \underline{g_m v_{be}} + g_{b'c} V_{ce} \quad | \quad i_b = 0 \quad \text{--- (1)}$$

$$i_c = h_{oe} V_{ce} \quad | \quad i_b = 0 \quad \text{--- (1)}$$

$$h_{oe} V_{ce} = V_{ce} g_{ce} + g_m v_{be} + g_{b'c} V_{ce} \quad | \quad i_b = 0$$

$\boxed{v_{be} = h_{re} V_{ce}}$


$$h_{oe} V_{ce} = \frac{V_{ce}}{r_{ce}} + g_m h_{re} V_{ce} + \frac{V_{ce}}{r_{b'c}}$$

$$g_{ce} = h_{oe} - g_m h_{re} - g_{b'c}$$


$$r_{ce} \approx 80 \text{ K}\Omega$$

iv)

$$\underline{V_{ce} = 0}$$

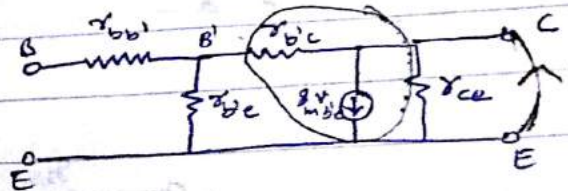

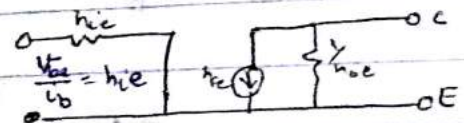
$$\frac{V_{be}}{i_b} = r_{bb'} + r_{b'e}$$






$$h_{ie} - r_{b'e} = r_{bb'}$$

$$\approx 100 \Omega$$

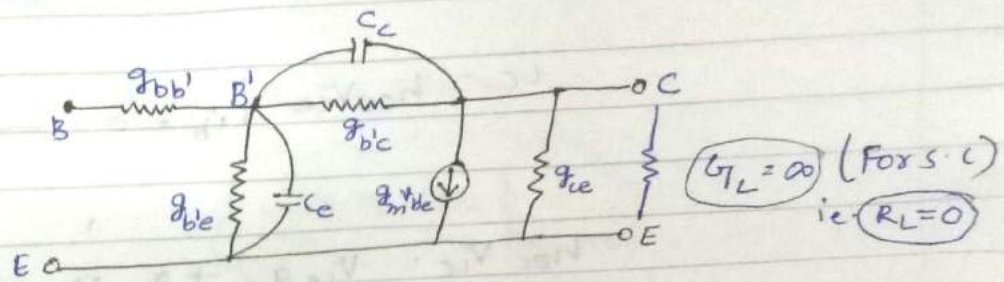S.C. current gain of BJT at high frequency :-



$$g_{bb'} \gg g_{b'e}$$

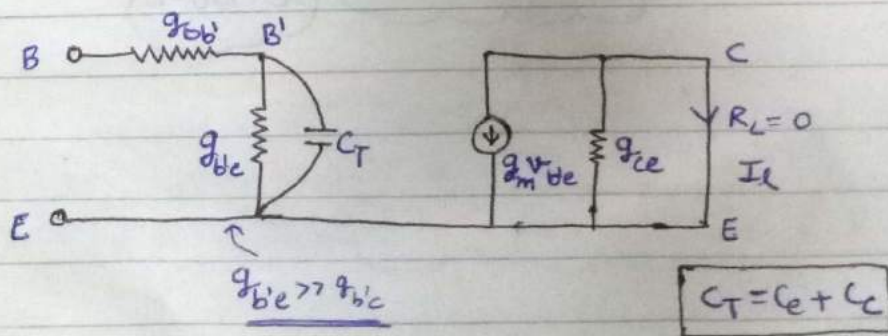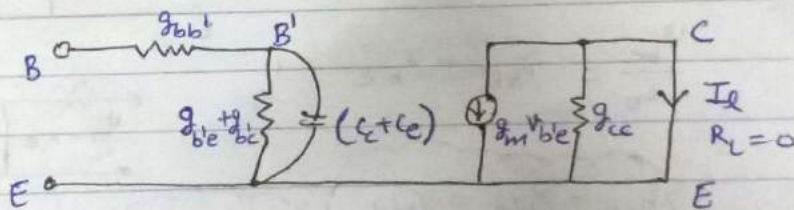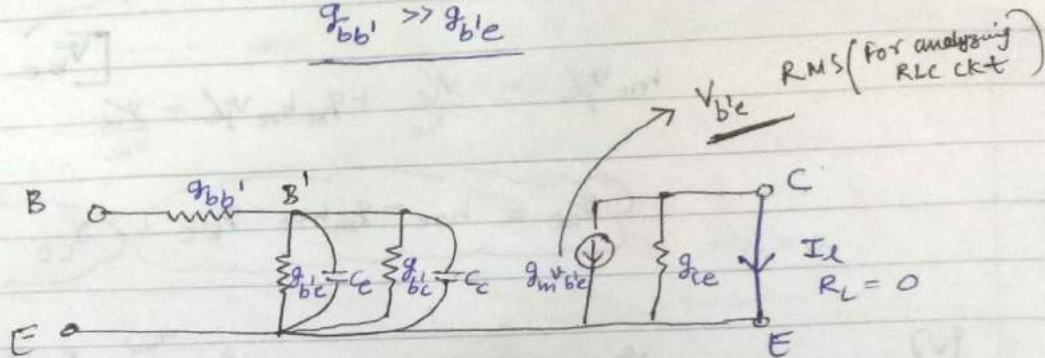

$$A_c = \frac{I_L}{I_i} \bigg|_{V_{ce}=0; R_L=0}$$

$$= \frac{-g_m V_{b'e}}{V_{b'e}} \rightarrow \{V_{b'e}\}_{RMS} \quad \left\{ Y = g_{b'e} + j\omega C_T \right\}$$


$$= \frac{-g_m}{g_{b'e} + j\omega C_T} \leftarrow \text{Remember}$$

$I_b = Y V_{b'e}$

$$\text{or } A_i = \frac{-g_m}{g_{b'e}} \cdot \frac{1}{1 + j\omega C_T g_{b'e}}$$

$$\text{or } A_i = \frac{-h_{fe}}{1 + j\omega C_T g_{b'e}}$$

$$|A_i| = \frac{h_{fe}}{\sqrt{1 + (2\pi f g_{b'e} C_T)^2}}$$

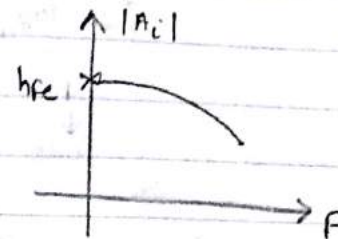

$$|A_i|_{\max} = h_{fe}$$

Now,

$$A_i = \frac{-h_{fe}}{1 + j\left(\frac{f}{f_\beta}\right)}$$

$$f_\beta = \frac{1}{2\pi g_{b'e} C_T}$$

f_β is { 3 dB freq.
cut off freq.
Half power point freq.
band width freq.

→ If h_{fe} is taken to be const

$$|A_i| = \frac{h_{fe}}{\sqrt{1 + \left(\frac{f}{f_\beta}\right)^2}}$$

$$f = 0; |A_i| = h_{fe}$$

$$f = f_\beta; |A_i| = \frac{h_{fe}}{\sqrt{2}}$$

* Power get reduced to half at $f = f_\beta$ i.e. if we ↑ the freq. upto f_β then power get reduced to half. Hence it is called half power point frequency.

* [0.707 times of max. is cut-off frequency → f_β]

* Amplifier is only working b/w $[0 - f_m]$.

* Amplifier gets cutoff beyond the frequency F_m according to IEEE standards.

* BW gets zero beyond the half power frequency.

$$20 \log_{10} |A_v| \text{ dB}$$


F
↓
0dB

F_B
↓
3dB

[If F_m has gone to max. from 3dB then we reject the amplifier]

—X—X—X—X—X—

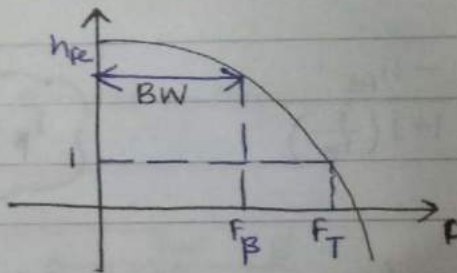- ∴ $[F_T \text{ is called unity gain Transition Frequency}]$



$$1 = \frac{h_{fe}}{\sqrt{1 + \left(\frac{F_T}{F_B}\right)^2}}$$

$$1 + \left(\frac{F_T}{F_B}\right)^2 = h_{fe}^2$$

$$\frac{F_T}{F_B} = \sqrt{h_{fe}^2 - 1}$$

$$\frac{F_T}{F_B} = h_{fe}$$


$$F_T = h_{fe} \times F_B$$

$$F_T = h_{fe} \times F_\beta = \text{Gain BW product}$$

$\downarrow$ $\downarrow$
 gain BW

* Gain BW product is always const.

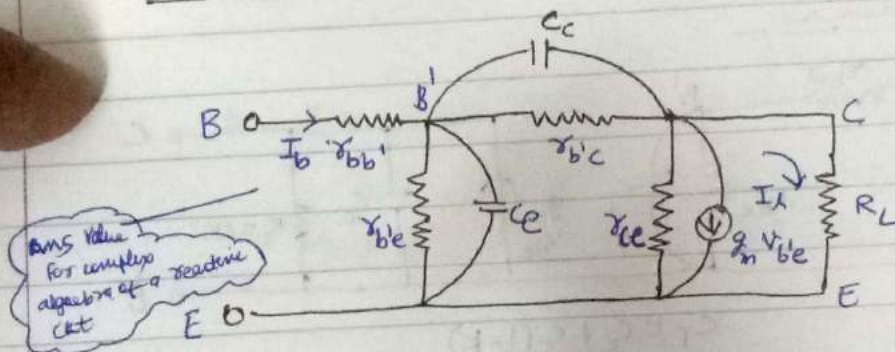
∴ To Find current gain of same BJT in presence of a Load :-



$$A_I = \frac{I_c}{I_b}$$

$$K = \frac{V_{ce}}{V_{be}}$$

By Millmann's Theorem :-

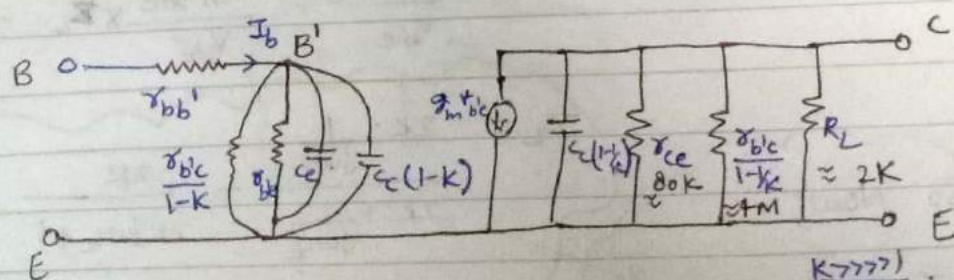


Wide band Amplifier
 $R_L \leq 2K$

$$C_c \left(1 - \frac{1}{K}\right) = C_c$$

$$r_{bc} \left(1 - \frac{1}{K}\right) = r_{bc}$$


Now R_L is dominate over r_{bc} & r_{ce} .

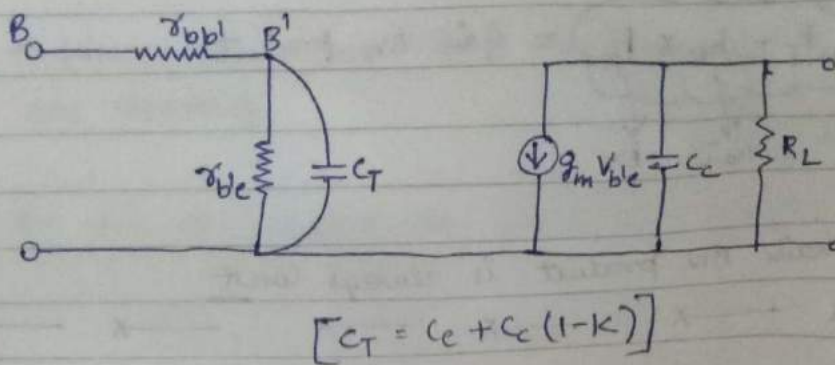& r_{be} is dominate over $\frac{r_{bc}}{1-K}$



— X — X — X — X — X —

Time Constant :-

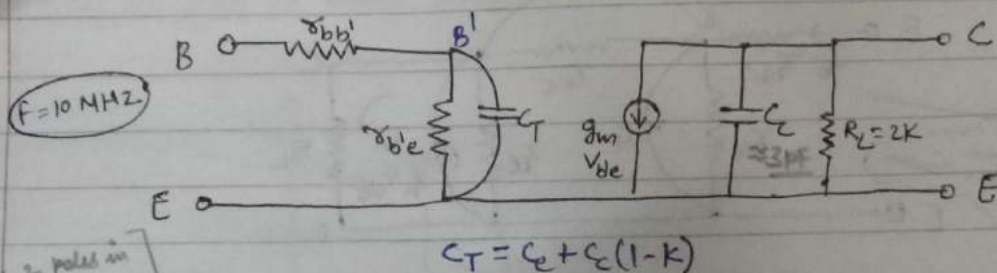

$Z_o = 2K \times 3\text{PF} = 0.1\text{P}$
 $\tau_o = 6\text{ns}$

$K = \frac{V_{ce}}{V_{be}} = \frac{-g_m V_{be}}{V_{be}} \times Z_L \approx -g_m Z_L$

$Z_L = \frac{2K \cdot \frac{1}{j\omega C_c}}{2K + \frac{1}{j\omega C_c}} = \frac{2K}{2Kj\omega C_c + 1} = \frac{2K}{\sqrt{1 + K^2 \omega^2 C_c^2}}$
 $= \frac{2K}{\sqrt{1 + 10^6 \times 10^6 \times 3 \times 10^{-12} \times 2 \times 10^3}}$
 $= \frac{2K}{\sqrt{1.14}}$
 $\approx 2K \approx R_L$

So Now;


$K = -g_m R_L$

$C_T = C_e + C_c(1-K)$

$$C_T = C_e + C_c (1 + g_m R_L)$$

$$= 100 + 3(1 + 100)$$

$$C_T \approx 403 \text{ pF}$$

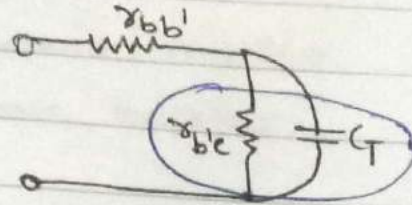

$$\tau = 403 \text{ pF} \times 1000$$

$$\tau_i = 403 \text{ ns}$$

* In these 2 time const; bigger one (τ_i) is dominant over smaller one (τ_o) because it take more time to stable.

$$f_B = \frac{1}{2\pi RC}$$

$$A_I = \frac{I_1}{I_b} = \frac{-g_m V_{b'e}}{V_{b'e} [g_{b'e} + j\omega C_T]}$$

$$A_I = \frac{-h_{fe}}{\left[1 + j\frac{f}{f_H}\right]}$$

where

$$f_H = \frac{1}{2\pi r_{b'e} (C_e + C_c (1 + g_m R_L))}$$

Hz