


Institute of Engineering and Technology
Devi Ahilya University, Indore
Mid Sem Test II November 2023

Class/Section : BE (IT) A & B Section
 Sub/Sub code : 1ETRC4- Basic Electronics

Max. Marks : 20
 Time : 1 hour

Note :: Attempt only 4 questions. All questions carry equal marks.

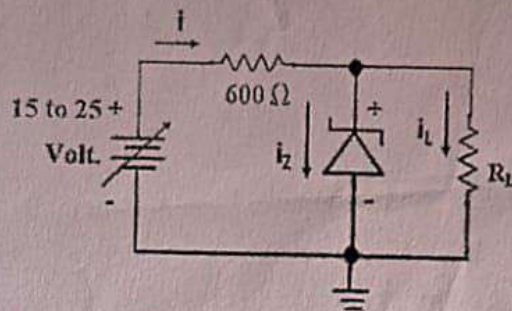- Q.1) (a) The Zener voltage of the Zener diode shown in figure is 12V. Find the Maximum and Minimum Currents. [3]



- (b) What are the differences between Zener breakdown and avalanche breakdown [2]

- Q.2) Describe the process of electron-hole recombination and how it relates to light emission in an LED. Also discuss the semiconductor material that contributes to the LED's. [5]
- Q.3) Explain fixed-biased with Emitter resistor and derive expression for operating point (V_{CE} , I_C). Why this circuit is thermally stable as compare self-biased without Emitter resistor. [5]
- Q.4) Draw circuit of Voltage divider biased, How to resolve in to equivalent circuit. Also calculate expression for operating point (V_{CE} , I_C). [5]
- Q.5) In the figure, assume that $V_{CC} = 9V$, $R_b = 360 K\Omega$, $R_c = 2K\Omega$, $\beta = 100$, $V_{be} = 0.7 V$, Calculate Q point (V_{CE} , I_C). construct dc load line and mention Q point on load line. [5]

