
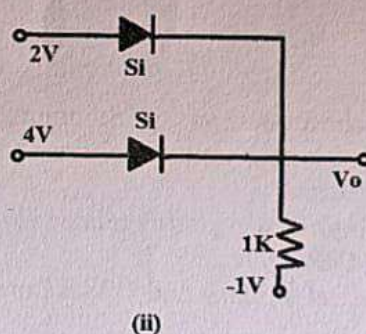


B.E. I YEAR EXAMINATION JANUARY 2024
1ETRC4- Basic Electronics
Information Technology (A &B)


M. Marks: 60

Note: Attempt any two parts from each question.

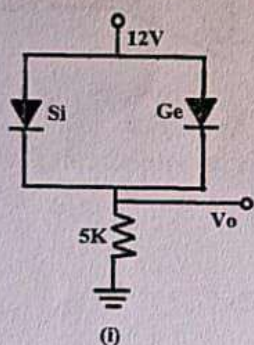
- Q1. a) How does the applied voltage across a PN junction affect the Fermi energy levels and the depletion region width? [6]
 b) Compare and contrast the impacts of temperature on the carrier mobility in intrinsic and extrinsic semiconductors, explaining the underlying mechanisms. [6]
 c) (i) Discuss the components required to obtain regulated DC power supply. [3]
 (ii) Calculate the reverse saturation current of a diode if the current at 0.2V forward bias is 0.1mA at a temperature of 25°C and the ideality factor is 1.5. [3]
- Q2. a) Find RMS value, Average value, Ripple factor, Efficiency and PIV of half wave rectifier. Also, compare the performance of half wave rectifier with and without filter. [6]
 b) Draw and explain VI characteristic of tunnel diode using fermi energy level diagram. [6]
 c) (i) Draw the ideal characteristics of diode and explain how it differs from that of a practical diode. [2]
 (ii) From the circuit diagram given in figure (i) and (ii) find V_o . [4]



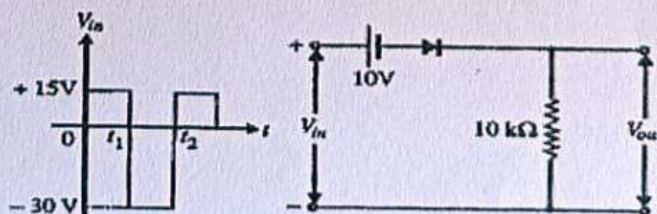
- Q3. a) Explain the working principal of NPN transistor. Also drive relations between α , β and γ (where α , β and γ are current gain in different transistor configurations). [6]
 b) For the circuit and input waveform given below, (i) Draw output waveform (ii) Find the peak value and expression for the output. [6]



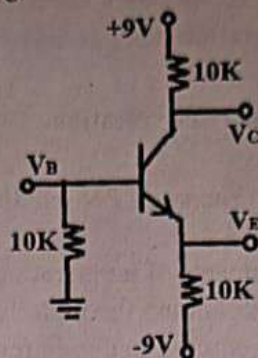- c) For the circuit shown below, measurement indicates the value $V_B = -1.5\text{ V}$, Assuming that $V_{BE} = 0.7\text{ V}$, Calculate V_E , β and V_C . [6]



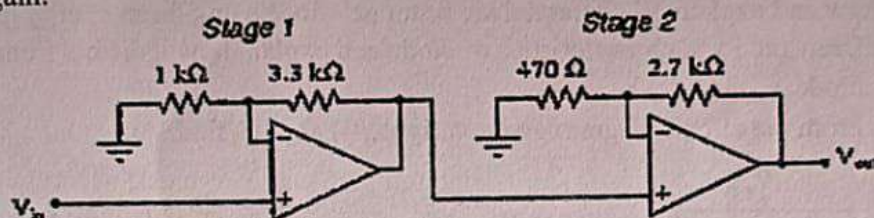- Q4. a) Explain the Ideal characteristics of Op-Amp (Operational Amplifier). [6]
 b) What do you mean by differential amplifier and Push-Pull Amplifier? Explain mechanism with circuit diagram. [6]
 c) Calculate the voltage gain for each stage of this amplifier circuit then also calculate the overall voltage gain. [6]



- Q5. a) Write short notes on: (i) Summer Amplifier (ii) Difference Amplifier [6]
 b) Describe logarithmic Amplifier and Anti-logarithmic Amplifier with circuit diagram and output expressions. [6]
 c) Explain following terms related to Op-Amp: [6]
 (i) CMRR (ii) Slew rate
 (iii) Offset Voltage and Offset Current (iv) Level Shifter