

BE Ist Year Test I (CS A & B)
IET-DAVV
Basic Electronics

Note: Attempt all questions carrying equal marks.

- Q1) Write a short note on full wave bridge rectifier. Also derive rms value, average value, ripple factor, form factor and peak factor. (10)
- Q2) An a.c. supply of 230 V is applied to a half-wave rectifier circuit through a transformer of turn ratio 10:1. Find (i) the output d.c. voltage and (ii) the peak inverse voltage. Assume the diode to be ideal. (10)