

Roll no.

2024249

BE 1st Year Examination, Jan 2024
BE 1st Year (CS A&B)
IETRC4: Basic Electronics

Duration: 3 hours

Max marks: 60


NOTE: Attempt any Two parts out of Three in each question. Take suitable assumption where needed.

Q1) A. Describe conduction in a p-n junction diode. Also explain its characteristics. (6)


B. Compare between insulator, conductor and semiconductor. (6)

C. When a reverse bias is applied to germanium p-n junction diode, the reverse saturation current at room temperature is $0.3\mu A$. Determine the current flowing in the diode when $0.15V$ forward bias is applied at room temperature. (6)

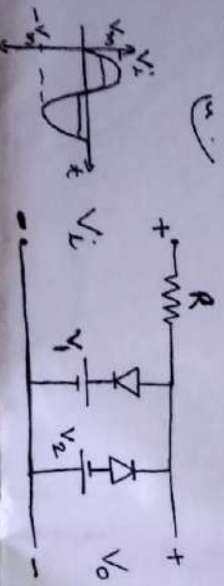Q2) A. Draw the output waveform for the following clipper circuit. (6)



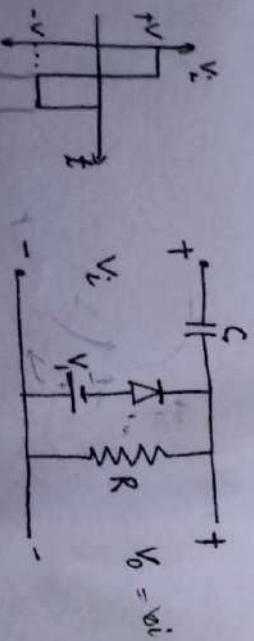B. Draw the output waveform of the clamper circuit. (6)



C. An a.c. supply of $230V$ is applied to a half-wave rectifier circuit through a transformer of turn ratio $10:1$. Find (i) the output d.c. voltage and (ii) the peak inverse voltage. Assume the diode to be ideal. (6)

Q3) A. Design a voltage regulator that will maintain an output voltage of $20V$ across a $1k\Omega$ load with an input that will vary between $30V$ and $50V$. That is, determine the proper value of R_s and the maximum current I_{zm} . (6)

B. Write short notes on the following. (3×2)

i) Varactor diode ii) Tunnel Diode (6)

C. Explain the working of Zener diode as voltage regulator with all three cases. (6)

Q4) A. Compare between CB, CE and CC configuration of an NPN transistor. (6)