

CLASS TEST # 3

ANALOG ELECTRONICS - 3ETRC4

B.E. 2nd YEAR (E & TC)

INSTRUCTIONS : Be precise and upto the mark , supplementary copies are not allowed.Each question is of 5 marks.

Max marks 20

1. Explain problem of biasing in High input impedance circuits.
2. Explain how can you solve biasing problem using an example.
3. Draw high frequency Pi model for BJT . Write down its salient features as compared to low frequency H parameter model
4. Derive the expression for short circuit transconductance gain g_m of a BJT .

Tear from this line