

Devi Ahilya University
Institute of Engineering & Technology, Indore
Class Test: I

Sub Code: 3ETRG1/3EIRG1

Class: II Year

Duration: 70 Min.

Note: All questions carry equal marks.

Sub Name: Network Analysis

Branch: E & TC (A and B Section)/EI

Maximum Marks: 20

- Q.1 Using Superposition theorem, determine the voltage V_0 as shown in fig 1. 5
- Q.2 Find Thevenin's equivalent circuit across the terminal AB and then find load current and power loss in 5Ω resistor for the network shown in fig. 2. 5
- Q.3 Explain Linear time invariant system. Also derive input-output relation. 5
- Q.4 Derive the formulae for coefficients of sine and cosine terms in first trigonometric form of Fourier series. 5

