

Sub Code: 3ETRG1/3EIRG1

Class: II Year

Duration: 70 Min.

Sub Name: Network Analysis

Branch: E & TC (A and B Section)/EI

Maximum Marks: 20

Note: All questions carry equal marks.

- Q.1 Using Star-Delta transformation find the current through the galvanometer as given in fig 1. 05
- Q.2 Capacitor is initially charged to voltage V_0 as shown in fig 2. At $t = 0$, switch K is closed. If $C_1 = C_2 = 1 \mu\text{F}$, $V_0 = 10 \text{ V}$ and $R = 10 \Omega$, find the (i) current $i(t)$ (ii) voltage across R and (iii) charge across C_1 after $t = 10 \mu\text{s}$. 05
- Q.3 Describe Fourier transform and its symmetric properties. 05
- Q.4 Find the Laplace transform of (i) $\sin \omega t$ and (ii) $e^{at} \cos \omega t$. 05

