
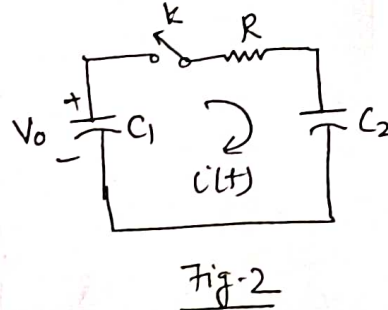


Sub Code: 3ETRG1/3EIRG1
Class: II Year
Duration: 70 Min.

Sub Name: Network Analysis
Branch: E & TC (A and B Section)/EI
Maximum Marks: 20

Note: All questions carry equal marks.

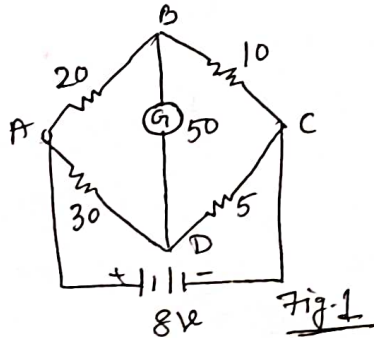- Q.1 Using Star-Delta transformation find the current through the galvanometer as given in fig 1. 05
- Q.2 Capacitor is initially charged to voltage V_0 as shown in fig 2. At $t = 0$, switch K is closed. If $C_1 = C_2 = 1 \mu F$, $V_0 = 10 V$ and $R = 10 \Omega$, find the (i) current $i(t)$ (ii) voltage across R and (iii) charge across C_1 after $t = 10 \mu s$. 05
- Q.3 Describe Fourier transform and its symmetric properties. 05
- Q.4 Find the Laplace transform of (i) $\sin \omega t$ and (ii) $e^{at} \cos \omega t$. 05




Devi Ahilya University
Institute of Engineering & Technology, Indore
Class Test: III

Sub Code: 3ETRG1/3EIRG1
Class: II Year
Duration: 70 Min.

Sub Name: Network Analysis
Branch: E & TC (A and B Section)/EI
Maximum Marks: 20

Note: All questions carry equal marks.

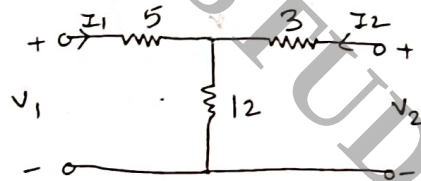- Q.1 Calculate the Z and Y parameters for the network given in fig. 1. 05



- Q.2 Solve the differential equation $\frac{d^2V}{dt^2} + 5\frac{dV}{dt} + 6V = e^{-2t} + 5e^{-3t}$ for $V(0+) = 1$ and $\frac{dV}{dt}(0+) = -1$ 05
- Q.3 Check the function for positive realness $F(s) = \frac{s+4}{s^2+2s+5}$ 05
- Q.4 Synthesis the network using Cauer I and II form if $Z(s) = \frac{s^4+7s^2+9}{s(s^2+4)}$ 05

Devi Ahilya University
Institute of Engineering & Technology, Indore
Class Test: I



Sub Code: 3ETRG1/3EIRG1
Class: II Year

Sub Name: Network Analysis
Branch: E & TC (A and B Section)/EI
Maximum Marks: 20

Duration: 70 Min.

Note: All questions carry equal marks.

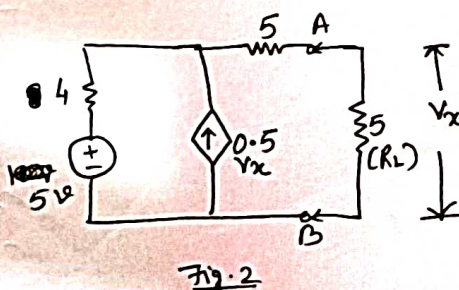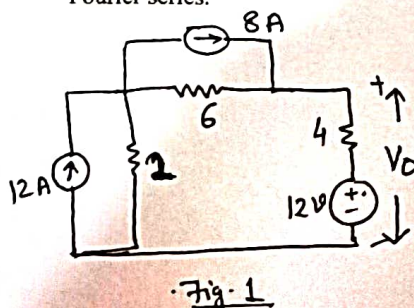- Q.1 Using Superposition theorem, determine the voltage V_0 as shown in fig 1. 5
- Q.2 Find Thevenin's equivalent circuit across the terminal AB and then find load current and power loss in 5Ω resistor for the network shown in fig. 2. 5
- Q.3 Explain Linear time invariant system. Also derive input-output relation. 5
- Q.4 Derive the formulae for coefficients of sine and cosine terms in first trigonometric form of Fourier series. 5




II B.E. EXAMINATION DEC- 2023
E & TC/ E & I ENGG.
3ETRG1/ 3EIRG1: NETWORK ANALYSIS

Duration: 3 Hrs.


Max. Marks : 60

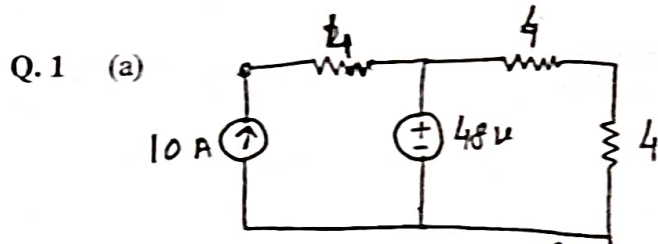Note: Attempt any two parts of each question. Each question carries equal marks. Make suitable assumptions if necessary.




Solve the network using (a) mesh analysis and (b) node analysis in Ideal condition.

6

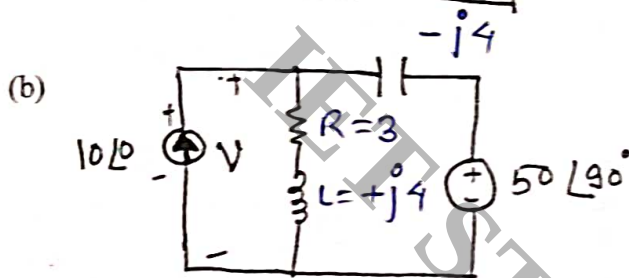


By Super-position theorem, find the voltage V in the given circuit.

6

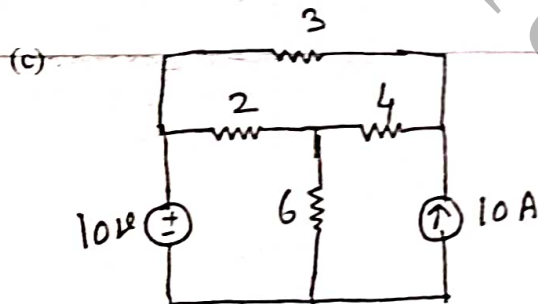


Find the current in 3Ω resistor using Norton's theorem.

6

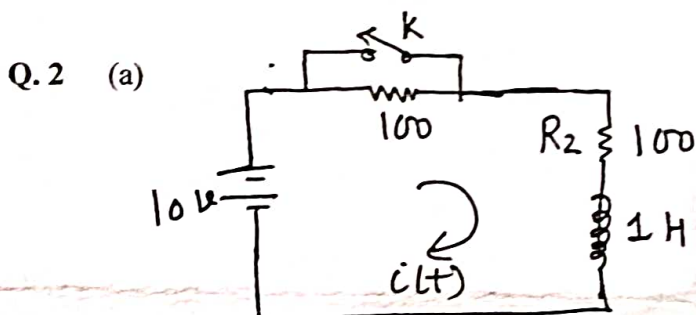

In the given network, the switch K is closed at $t=0$. Find (i) $i(t)$, (ii) V_{R2} and (iii) V_L the voltage across the inductor, at $t=5\text{ msec}$

6

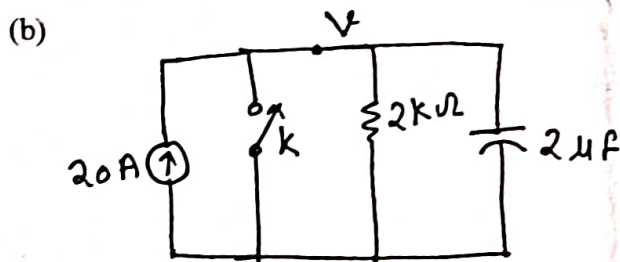

Switch K is opened at $t=0$ with zero capacitor voltage. Find (i) V (ii) dV/dt and (iii) d^2V/dt^2 at $t=0+$.

6

$$\frac{d^2V}{dt^2}$$

- (c) Solve the equation if $\frac{d^2v}{dt^2} + 3\frac{dv}{dt} + 2v = 10 \sin 10t$ for $v(0+) = 1$ and $dv/dt(0+) = -1$ 6


Q. 3 (a) Check the stability of the network functions whose characteristic equations are given by: 6

(i) $s^4 + 11s^3 + 2s^2 + 3s + 2 = 0$

(ii) $s^5 + 3s^4 + 3s^3 + 4s^2 + s + 1 = 0$


Also find no. of roots to left side of, on the and to the right side of, imaginary axis in each case.

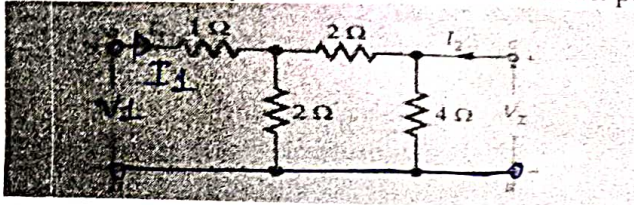(b) Determine the Z parameters and Transmission parameters for the network shown below 6




(c) Discuss and derive the condition of symmetry and reciprocity in terms of Z parameters and H (Hybrid) parameters. 6

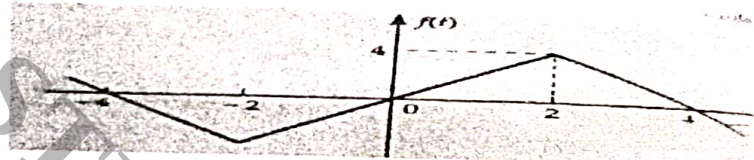Q. 4 (a) Obtain the Fourier series expansion in trigonometric form 1 and form 2, for the waveform shown in the Fig. below; 6



(b) Explain and derive Initial value theorem, Final value theorem and linear convolution theorem in context to Laplace Transforms of time domain functions. 6

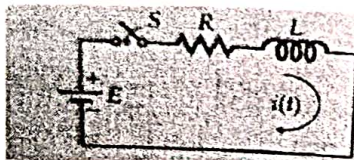(c) Determine the response of series R L circuit shown below for DC supply of E volt, using Laplace transform; 6



Q. 5 (a) Discuss the properties of Positive Real Network Functions. Check the Positive realness of the function given by; 6

$$Z(s) = \frac{s^3 + 3s^2 + 9s + 3}{s^3 + 4s^2 + 7s + 9}$$

(b) Synthesize the network using Cauer I and II form if function is $Y(s) = \frac{(s^2+1)(s^2+5)}{s(s^2+3)}$ 6

(c) Synthesize the network using Foster I and II form if function is $Z(s) = \frac{(s^2+1)(s^2+4)}{s(s^2+2)}$ 6

CLASS TEST #2

Analog Electronics : 3ETRC4

B.E 2ND YEAR (ELECTRONICS AND TELECOMMUNICATIONS)

Instructions : Attempt all questions . Each question carry 05 marks. Do not use unfair means like copying and cheating. Supplementary copies are not allowed. Time limit as per exam rules.

1. Write down typical H parameter values of common emitter, common base and common collector configuration as given in table 8.2 of your text book.
2. Derive general expressions for current gain and voltage gain using H parameter model of a typical transistor based amplifier.
3. Explain Miller's theorem and prove it.
4. What is Thevenin's and Norton's method of finding output impedance of any amplifier. Justify your method by finding out its expression.

-----CUT FROM HERE-----

CLASS TEST # 3

ANALOG ELECTRONICS - 3ETRC4

B.E. 2nd YEAR (E & TC)

INSTRUCTIONS : Be precise and upto the mark , supplementary copies are not allowed. Each question is of 5 marks.

Max marks 20

1. Explain problem of biasing in High input impedance circuits.
2. Explain how can you solve biasing problem using an example.
3. Draw high frequency Pi model for BJT . Write down its salient features as compared to low frequency H parameter model
4. Derive the expression for short circuit transconductance gain g_m of a BJT .

-----Tear from this line-----

INSTITUTE OF ENGG. AND TECHNOLOGY, DAVV

B.E 2nd YEAR ,ELECTRONICS AND TELECOMMUNICATIONS(DEC 2023)


ANALOG ELECTRONICS (3ETRC4)

TIME 3HRS

MAX MARKS 60

NOTE: ATTEMPT ANY TWO PARTS FROM EACH QUESTION. EACH QUESTION IS OF 12 MARKS AND EACH PART IN IT IS OF 06 MARKS. BE PRECISE AND UPTO THE MARK. MAKE SUITABLE ASSUMPTIONS IF NEEDED AND MENTION IT EXPLICITLY. PARTS OF THE SAME PROBLEM MUST BE SOLVED IN CONTINUATION.

- 1 (A) Find the exact expression for h_{fe} in terms of common base H parameters at low frequencies. From this exact relation obtain approximate expression for h_{fe} .
- (B) Find the exact expression for h_{rb} in terms of common emitter H parameters at low frequencies. From this exact relation obtain approximate expression for h_{rb} .
- (C) For the composite transistor shown below. Derive expression for h'_{ie} for this composite transistor using original H parameters.

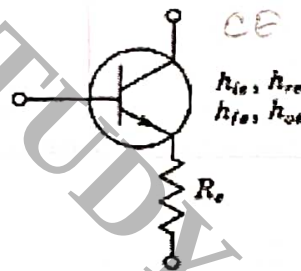


- 2 For the amplifier in the circuit shown below. Take $R_s = 0.1 \text{ kohms}$ and $R_L = 5 \text{ kohms}$. Use standard values of H parameters.

12

Find out

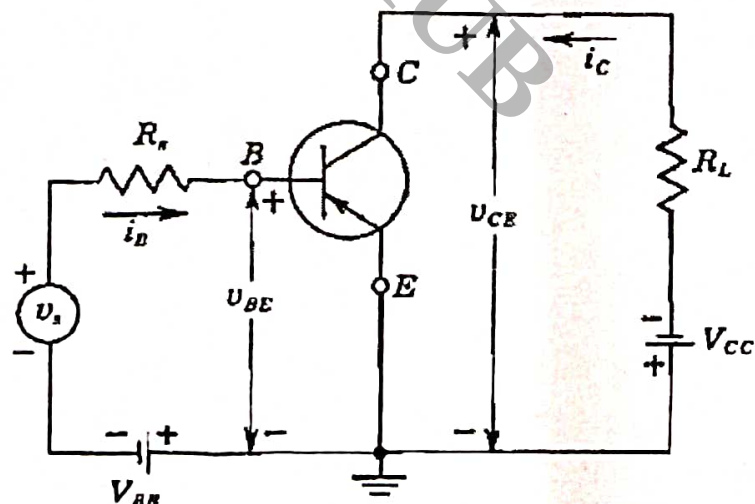- (A) Current gain A_i
- (B) Voltage gain A_v
- (C) Input impedance R_i



3 (A) Derive expression for Input impedance of Darlington's circuit .

(B) Explain the problem of biasing in High input impedance circuits using an example.

(C) Explain method of Bootstrapping to solve biasing problem.

4 (A) Draw Giacolleto model of Bipolar junction transistors. Write down values of its parameters at $I_{CQ} = 1.3 \text{ mA}$.

(B) Derive expression for g_m at high frequencies for a bipolar junction transistor.

(C) Derive expression for hybrid Pi capacitance C_e .

5 (A) Derive expression for f_β and explain the meaning of f_T . Establish a relation between them.

(B) Draw schematic block diagram of negative feedback based amplifier system. Explain its various components.

(C) Explain phase shift oscillator in full detail.

Class Test I August 2023
2nd Year Electronics & Telecomm Engg. (Section A & B)
3ETRC3 Data Structure

Time: 70 min

Max Marks: 20

Note: 1. Attempt any four questions. All questions carry equal marks.

2. Write the output with sample input while answering programming question

- Q.1 Write C program to add two integers using functions and pointers.
- Q.2 Define Data Structures. What are different types of data structures?
- Q.3 What all operations are possible on Data Structures? Explain in brief.
- Q.4 Write a C program for inserting an element in 1D array other than last position.
- Q.5 For 2D array declared as: `int arr[][2]={1,2,3,4};`
- i. draw the memory map for row major format.
 - ii. find out size of array in Bytes.
 - iii. find out number of rows.
 - iv. find out number of elements in array.
 - v. for base address =1000, find out address of `arr[1][1]`.

2nd Year Electronics & Telecomm Engg. (Section A & B)
3ETRC3 Data Structure

Time: 70 min

Max Marks: 20

Note: 1. Attempt any four questions. All questions carry equal marks.

2. Write the output with sample input while answering programming question

Q.1 Write C program to find the number = 23 in the following data set using Binary Search algorithm.
Data[] = {5, 7, 9, 21, 23, 35, 78, 89, 93, 98}

Q.2 Illustrate the quick sort algorithm to sort the following data set.
Arr[] = {30, 52, 29, 87, 63, 27, 19, 54}

Q.3 What are the various applications of stack and queue. Explain in brief.

Q.4 Convert the following expression to Polish and Reverse Polish notation:
Expression: $a + (b * c + d) / e$

Q.5 How Circular queue overcomes limitation of linear queue? Write the algorithm for Insertion and Deletion in a circular queue

Exam Code:2024034

BE 2nd Year Examination
December 2023
Electronics and Telecommunication (Section A & B)
3ETRC3 DATA STRUCTURE


Time: 3 Hrs

Max.Marks: 60


- Note: 1. Attempt any 2 parts of each question, all questions carry equal marks.**
2. Write the output with sample input while answering programming question.
3. Attempt both the parts of question at same place.

- 1 a) Define Data Structures. How are they different from data types? What are different types of data structures?
- b) Consider a two-dimensional array declared as:
`int marks[ ][5]={50,70,50,45,62,84,65,45,74,70,98,45,65,86,38};`
i. Draw the memory map for row major format.
ii. Find out the size of array in Bytes.
iii. Find out the number of rows.
iv. Find out the number of elements in the array.
v. For base address =1000, assuming 4Bytes for "int" data type, find out address of marks[2][3].
- c) Compare Linear Search and Binary Search.
Write C program to find the number = 23 in the following data set using Binary Search algorithm.
`int Data[] = {5,7,9,21,23,35,78,89,93,98};`
- 2 a) Convert the following expression to Reverse Polish notation: (Mention all the steps by using the stack)
Expression: $A - (B / C + (D \% E * F) / G) * H$
- b) Present the algorithms for PUSH() and POP() operation over the STACK(to be implemented as linked list).
- c) Illustrate the quick sort algorithm to sort the following data set.
`int Arr[] = {30,52,29,87,63,27,19,54};`
- 3 a) How Circular queue overcomes limitation of linear queue? Write the algorithms for insertion and deletion in a circular queue. (implemented as array)
- b) Compare and Contrast, Linked List and Arrays. With the help of an example, illustrate creation of singly linked list.
- c) Form a binary max heap and binary min heap for the following data items:
50,40,35,25,20,27,33,58,10
- 4 a) i. Considering the in order and post order traversals, construct the binary tree:
In order: 10 15 20 23 25 30 35 39 42
Post order: 15 10 23 25 20 35 42 39 30

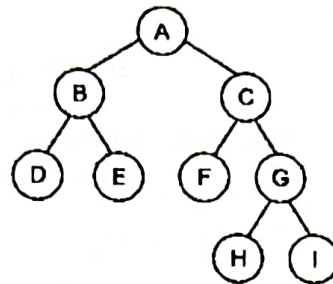- ii. For the following binary tree, find the in order, pre order and post order traversals




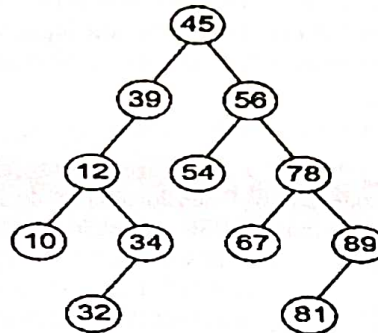- b) For the Binary Search Tree given below:
 i. Delete the root node
 ii. Insert 11,22,33,44,55,66,77




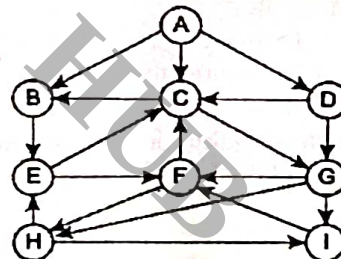- c) Create an AVL Tree using the following sequence:
 16, 27, 9, 11, 36, 54, 81, 63, 72

- 5 a) i. Define Graphs. What are applications of graph data structure?
 ii. How are graphs represented? Give the sequential and linked representation of a directed graph.
 b) What is meant by Graph Traversal? Find DFS and BFS for the following graph.



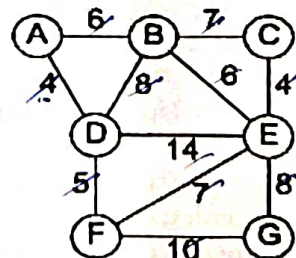- c) Construct the minimum spanning tree using:
 i. Prim's Algorithm with start Vertex D
 ii. Kruskal's Algorithm



II B. E (Electronics & Telecommunication)
Class Test III November 2023
Sub: 3ETRC2 Digital Electronics

Time: 70 min

Max Marks: 20

Note: Attempt any four questions. All questions carry equal marks.

- Q.1 Explain the working of negative edge triggered J-K flip-flop with the help of diagram containing negative edge detector circuit. 5
- Q. 2 Design a digital circuit to convert RS flip-flop to T-Flip-flop. 5
- Q. 3 Design a positive edge triggered mod-5 asynchronous counter using T-flip-flop. Also draw the timing diagram at output of all flip-flops. 5
- Q. 4 A 5 bit switched current DAC has an output of 10mA for a digital input of 10100. What will be the output current for an digital input of 11010? 5
- Q.5 Design an A/D converter of 3 bit with maximum analog voltage of 7.0 V. The maximum quantization error allowed is $\pm 0.5V$. Also determine the input voltage at negative terminal of the comparators. Make suitable assumptions. 5

II B. E (Electronics & Telecommunication)
December 2023 Examination
Sub: 3ETRC2 Digital Electronics

2024033

Time: 3 hrs.

Max Marks: 60

Note: Attempt all five questions. Attempt any two part of each question. All questions carry equal marks.

- Q.1 a) (i) Determine the value of base r_1 and r_2 , if $(121)_{r_1} = (100)_{r_2}$ and $(34)_{r_1} = (41)_{r_2}$. Base of the numbers r_1 and r_2 are positive integers. 3
- a)(ii) Perform following subtraction using 2's complement (8 bit number) subtraction $68 - 95$. Also give answer in 8 bit 2's complement form. 3
- Q.1 b) (i) A code has four-bit code word has following valid codes. 0001,0010,0100,0111,1000,1011,1101,1110. How many errors can be detected in this code? Give reason for your answer. 3
- b)(ii) Following sequence is received at the receiver of a system. 1010 0110 1011.
It is given that the sequence contains 8 bit of message and coded in Hamming code. Determine message. (Correct it if required.) 3
- Q.1 c) (i) What are open collector gates? Explain the concept of Wired AND operation. 3
- c) (ii) Draw and explain the working CMOS Inverter gate. 3
- Q.2 a)(i) Obtain the minimal expression in SOP form for $F(a,b,c,d) = \sum m(0,1,2,3,5,7,8,9,11,14)$ using K-Map method. Draw the NAND-NAND circuit. 3
- a)(ii) Using K-map method obtain NOR-NOR circuit for following function and draw the circuit.
 $F(a,b,c,d) = \pi M(1,4,6,9,10,11,14,15)$ 3
- b)(i) Prove that.
 $((AB' + ABC)' + A(B + AB'))' = 0$ 3
- b)(ii) Prove that if $AB' + A'B = C$, then $AC' + A'C = B$ 3

P.T.O.

- c)(i) Implement the following multiple output combinational circuit using a 3 line to 8 line decoder.
 $F_1 = \sum m(0,1,5,7)$
 $F_2 = \sum m(2,5,6,7)$
 $F_3 = \sum m(0,3,4,6)$ 3
- c(ii) Implement following expression using appropriate multiplexer. 3
 $f_1(a,b,c,d) = \sum m(0,2,3,6,8,9,12,14)$
- Q.3 a) Design a full adder circuit using only NAND gates. Also draw the circuit. 6
 b) Design negative edge triggered T-flip-flop with an active low PRESET and CLEAR asynchronous input. 6
 c) Design a four-bit parity generator circuit. Also design a parity checker circuit to check the output generator circuit. 6
- Q.4 a) Design a negative edge triggered mod-13 asynchronous up counter using JK-flip-flop. 6
 b) Design a synchronous counter goes through states 0, 5, 4, 2, 0... Is this counter self-starting? Use negative edge triggered T flip-flops. 6
 c) Design a combinational circuit to convert a R-S flip-flop to T-flip-flop. 6
- Q.5 a) Explain working 4 bit switched current source type D/A converter. If logic 1 = 5V and Logic 0 = 0V, then determine analog value of digital input 1010. 6
 b) An 8-bit successive approximation type ADC has resolution of 10 mV. What is the digital output for analog value 1.62V 6
 c) Design a Schmitt trigger circuit using 555 timer IC. 6

IET, DAVV, Indore
B.E. II (ETC)
Class Test II (Oct 2023)
3ATR2C1: Applied Mathematics-III

Time: 70 min

Max Marks: 20

Note: Attempt any FOUR questions. All questions carry equal marks.

Q.1. Find the Taylor's and Laurent's series which represents the function $f(z) = \frac{(z-2)(z+2)}{(z+1)(z+4)}$, (05)

In the regions: (i) $|z| < 1$, (ii) $1 < |z| < 4$, (iii) $|z| > 4$.

Q.2. Find the residue of the function $f(z) = \frac{z^2 - 2z}{(z+1)^2(z^2+4)}$ at each pole. Using Residue theorem, (05)

evaluate $\int_C f(z) dz$, where $C: |z| = 1.5$.

Q.3. State Cauchy's integral theorem and evaluate the integral by using Cauchy's Integral (05)

Formula $\int_C \frac{4-3z}{2(z-1)(z-2)} dz$ where C is the circle $|z| = 3/2$.

Q.4. Evaluate $\int_0^1 \frac{dx}{1+x}$ using (i) Trapezoidal rule (ii) Weddle's rule. ($N = ?$) (05)

Q.5. Find the value of $f(8)$ for the given set of discrete data. (05)

X:	4	5	7	10	11	13
F(x):	48	100	294	900	1210	2028

IET, DAVV, Indore
B.E. II (ETC)
Class Test III (Nov 2023)
3ATR2C1: Applied Mathematics-III

Time: 70 min

Max Marks: 20

Note: Attempt any FOUR questions. All questions carry equal marks.

Q.1. Two telecom companies, Provider A and Provider B, are competing for subscribers. Provider A's customer exhibit a 85% loyalty rate, while 60% of Provider B's former customers switch back to Provider A's service. (05)

- (i) Develop a state transition matrix illustrating customer movement between the two providers.
- (ii) Determine the probability that a customer will be using Provider A's service after two periods if they initially started with provider B.

Q.2. Test whether the following matrices are regular stochastic matrices: (05)

$$A = \begin{bmatrix} 0 & 1 \\ 1/2 & 1/2 \end{bmatrix}, \quad B = \begin{bmatrix} \frac{1}{2} & \frac{1}{2} & 0 \\ \frac{1}{2} & \frac{1}{2} & 0 \\ \frac{1}{4} & \frac{1}{4} & \frac{1}{2} \end{bmatrix}$$

PTO

B.E. II EXAMINATION DEC.' 2023
E&TC Engineering
3ATRC1: Applied Mathematics-III

Time: 3 Hrs.]

[Max. Marks: 60]

Note: Attempt any TWO parts from each Question. Each carries equal marks.

Q.1. (a) Find the Nature of Singularities for the following functions. (06)

i) $f(z) = \frac{\sin z}{z}$ ii) $g(z) = \frac{e^{1/z}}{z^2}$ iii) $u(z) = \frac{e^{2z}}{(z-1)^4}$

(b) If $f(z_1) = \oint_C \frac{3z^2+7z+1}{z-z_1} dz$ where C is the circle $x^2 + y^2 = 4$, find the value of (06)

(i) $f(3)$, (ii) $f'(1-i)$, (iii) $f''(1-i)$.

(c) Find Laurent expansion for $f(z) = \frac{7z-2}{z^3-z^2-2z}$ in the region given by (06)

i) $0 < |z+1| < 1$, ii) $1 < |z+1| < 3$, iii) $|z+1| > 3$.

Q.2. (a) The transition matrix P of the markov chain is as, (06)

$$P = \begin{bmatrix} 0 & \frac{1}{2} & \frac{1}{2} \\ \frac{1}{2} & \frac{1}{2} & 0 \\ 0 & 1 & 0 \end{bmatrix}$$

Initial probability distribution $P(0) = [2/3, 0, 1/3]$, if p_{ij} denotes m^{th} step transition probability, find $P^{(4)} \cdot P_{13}^{(2)}$, $P_{32}^{(2)}$.

(b) An electronic system comprises 6 silicon transistors, 4 germanium diodes, 8 film resistors, and 3 tantalum capacitors connected in a parallel circuit. Each component has its hourly failure rate: (06)

1. Silicon transistor: $\lambda = 6 \times 10^{-5}$
2. Germanium diodes: $\lambda = 2 \times 10^{-5}$
3. Film resistors: $\lambda = 1.5 \times 10^{-4}$
4. Tantalum capacitors: $\lambda = 1.8 \times 10^{-4}$

Calculate the reliability of the circuit for 10 hours, when the components follow exponential distribution.

(c) A Traveler visits one of three cities X, Y, and Z every day, never visiting the same city on consecutive days. If the traveler visits city X, the next day they visit city Y. If the traveler visits either city Y or Z, the next day they are twice as likely to visit city X as to visit the other city. If the traveler visits city Z on a Monday, what is the probability that they visit city X on the following Friday? For X, Y and Z: (06)

$$P = \begin{bmatrix} 0 & 1 & 0 \\ 2/3 & 0 & 1/3 \\ 2/3 & 1/3 & 0 \end{bmatrix}$$

Q.3. (a) (i) Evaluate $\int_0^4 e^x dx$ by Simpson's rule given that (06)

$e = 2.72$, $e^2 = 7.39$, $e^3 = 20.09$, $e^4 = 54.6$.

(ii) Use Trapezoidal rule to evaluate $\int_0^1 x^3 dx$ considering 5 sub-intervals.(b) Use Stirling's formula to evaluate $f(32)$ given that (06)

x	20	25	30	35	40
F(x)	14.035	13.674	13.257	12.089	11.309

- (c) Using Newton's divided difference formula, find $f(1)$. (06)

x:	-4	-1	0	2	5
F(x):	1245	33	5	9	1335

- Q.4. (a) Solve the system of equations by Gauss-Seidel iterative method correct to 2 decimal places. (06)

$$\begin{aligned} 54x + y + z &= 110, \\ 2x + 15y + 6z &= 72, \\ -x + 6y + 27z &= 85. \end{aligned}$$

- (b) Apply Runge-Kutta method (fourth order), to find an approximate value of y when $x = 2.0$, given that $\frac{dy}{dx} = x + y^2$ and $y(0) = 1$. [Interval $h = 0.1$] (06)

- (c) Find real root of equation $x^4 - x = 9$, by Newton-Raphson method correct to 3 decimal places. (06)

- Q.5. (a) (i) Write Dirichlet's conditions for Fourier series. (03)
(ii) Express the function $f(x)$ as Fourier integral. (03)

$$f(x) = \begin{cases} 1, & |x| \leq 1 \\ 0, & |x| > 1 \end{cases} \quad (03)$$

- (b) Find the Fourier half-range cosine series of the function (06)
- $$f(x) = \begin{cases} 2t, & 0 < t < 1 \\ 2(2 - t), & 1 < t < 2 \end{cases}$$

- (c) Find the Fourier series corresponding to the function $f(x)$ defined in $(-2, 2)$ as follows (06)

$$f(x) = \begin{cases} 2, & -2 \leq x \leq 0 \\ x, & 0 < x < 2 \end{cases}$$

I ET DAVV INDORE

Class Test 1 BE II year (EI / E&TC& MECH) AUG. 2023

(3SERS3/3STRS3/3SMRS3)Effective communication skill

TIME: 70 MIN

Max marks: 20

- Q.1 How can a person use good interpersonal communication skills? Write any 10 points (10)
- Q.2 How far the knowledge of cross culture helps at workplace? Write logically.(05)
- Q.3 What are the ways to improve your spoken English? (05)

- placement
- speech
- accent
- motivation
- apology
- teaching

I ET DAVV INDORE

Class Test II BE II year (EI /E&TC& MECH) OCT. 2023

(3EIRS3/3ETRS3/3EMRS3)Effective communication skill

TIME: 70 MIN

Max marks: 20

- Q.1 What are the advantages and disadvantages of on-line communication in teaching and learning ? (10)
- Q.2 What are the barriers to listening, also write the ways to remove them.(05)
- Q.3 Write the importance of listening in different spheres of life. (05)

2024037

IET DAVV

B.E.II YEAR Examination Dec.23

(3STRS3) Effective Communication Skills. (E&TC A&B)

Duration:3 hrs.

Max Marks:60

Q.1. Answer any one of the following:.

(a) What are the basic forms of communication? Write the process of communication with diagram? (12). (Or)

(b) What problems the students face, due to their weakness in speaking and writing English. Write in detail. (12)

Q.2 Answer any one of the following:.

(a) Write 10 points to build positive impression at the workplace. (12) (Or)

(b) Discuss the do's and don'ts for telephone communication in professional field. (12)

Q.3. Answer any one of the following:.

(a) How far listening helps in speaking skill? Write the barriers to listening and the ways to remove them. (12). (Or)

(b) Listening is the base for any communication. How can it improve one's personality? (12)

Q.4 Answer any one of the following:.

(a) Write 10 probable questions and answers for a job interview. (12). (Or)

(b) Make an evaluation table of skills, generally judged in an interview. (12)

Q.5 Answer any one of the following:.

(a) What is group discussion? Write in detail what strategy one should adopt to crack it. (12) (Or)

(b) What is audience analysis? What is its importance for presentation. (12)