





Digital Circuits and Systems

Multiplexers

Multiplexers

- *Multiplexing* means transmitting a large number of information units over a smaller number of channels or lines.
- A *digital multiplexer* (**MUX**) selects binary information from one of many input lines and directs it to a single output line.
 - Data selector($2^n:1$ MUX).
 - Inputs: 2^n data inputs, n select lines.
 - Output: 1 data output line.

<i>s1</i>	<i>s0</i>	<i>Out</i>
0	0	<i>D0</i>
0	1	<i>D1</i>
1	0	<i>D2</i>
1	1	<i>D3</i>

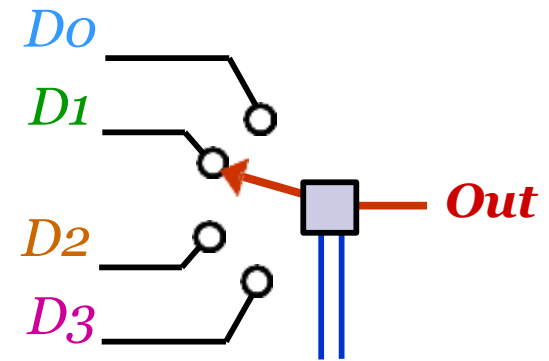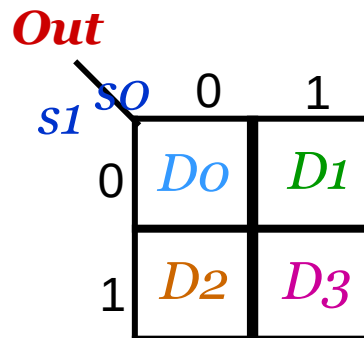

APPLICATIONS OF MULTIPLEXER


❑ **Communication System:**

- ❖ A communication multiplexer.
- ❖ By using a multiplexer, the efficiency can be increased.



❑ **Computer Memory:**

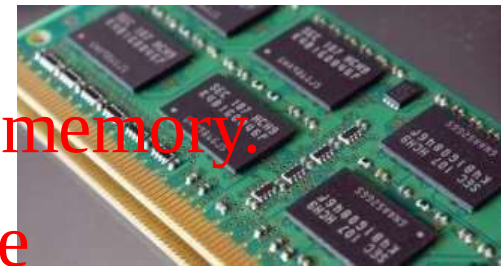- ❖ Multiplexers are used in computer memory.
- ❖ Reduces copper lines to connect the memory to other parts of the computer.




Telephone Network:

- ❖ In telephone networks, multiple audio signals are integrated.


Transmission from the computer of a satellite

Multiplexer is used to transmit the data signal. # from satellite to ground.
by using GSM satellite.

Functional Diagram Of a Multiplexer

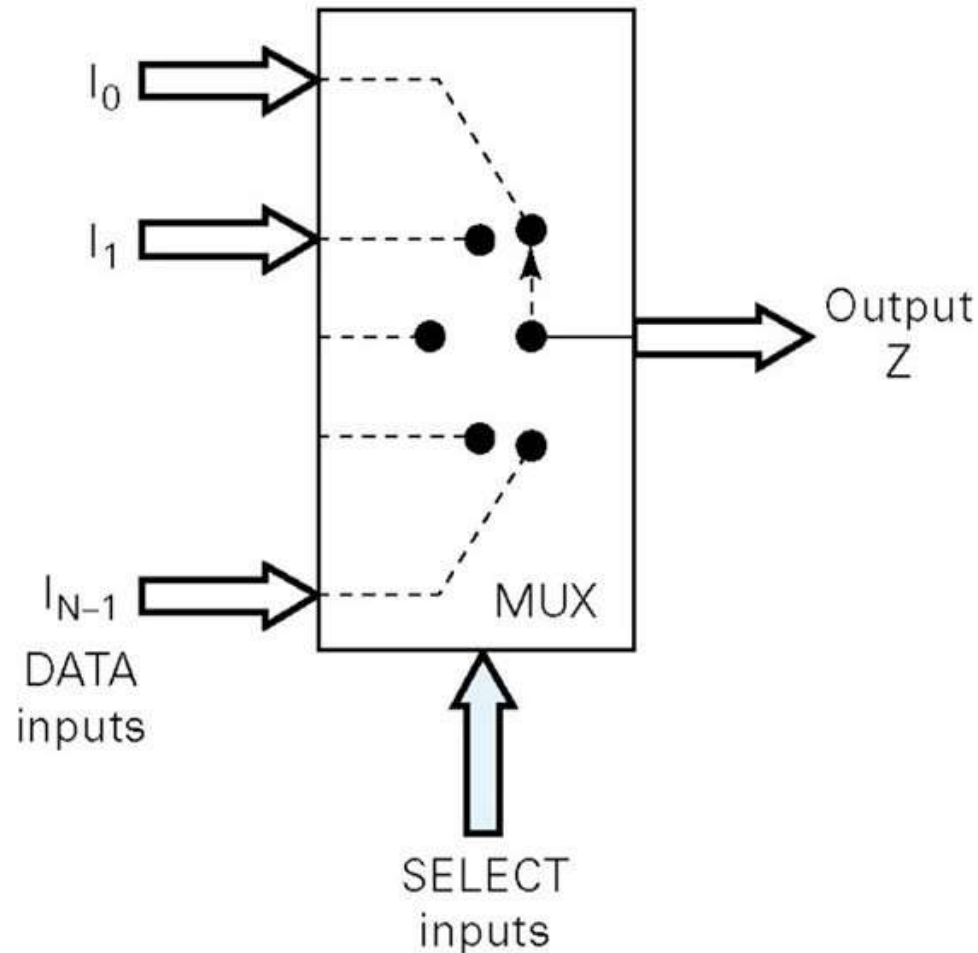


2:1 Mux

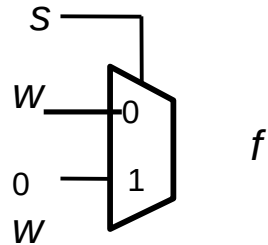

(a) Graphical symbol


s	f
0	w_0
1	w_1

(b) Truth table

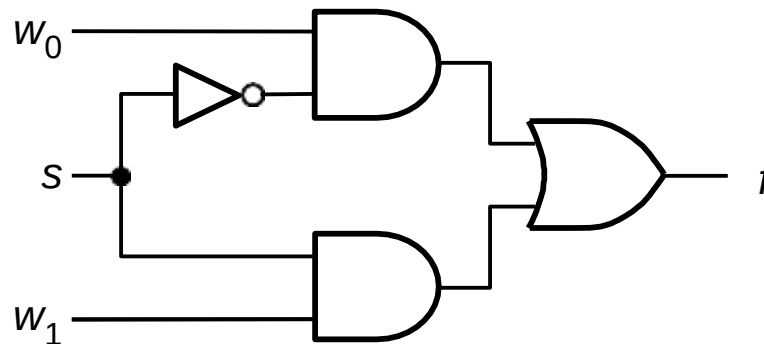

(c) Sum-of-products circuit

4 : 1 Multiplexer

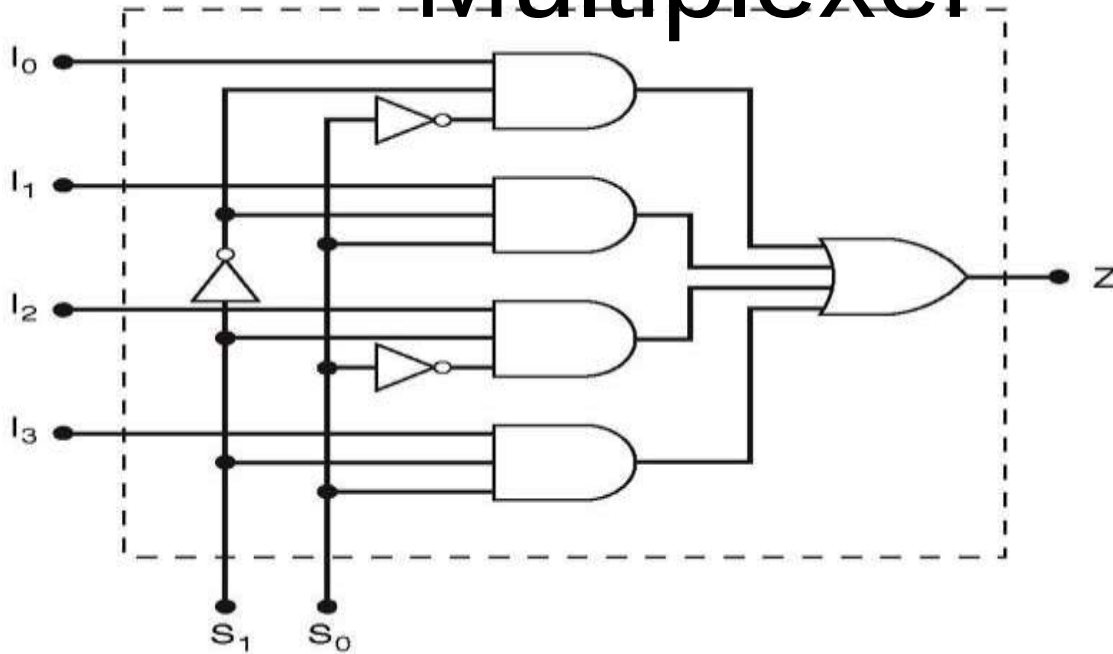


S_0	S_1	Z
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

- A $2^n:1$ MUX needs 2^n , $(n+1)$ -input AND gates for selection and a 2^n -input OR gate to generate the final output.
- $\Rightarrow$ *AND/OR logic structure*

S_0	S_1	Z
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

8 : 1 Multiplexer

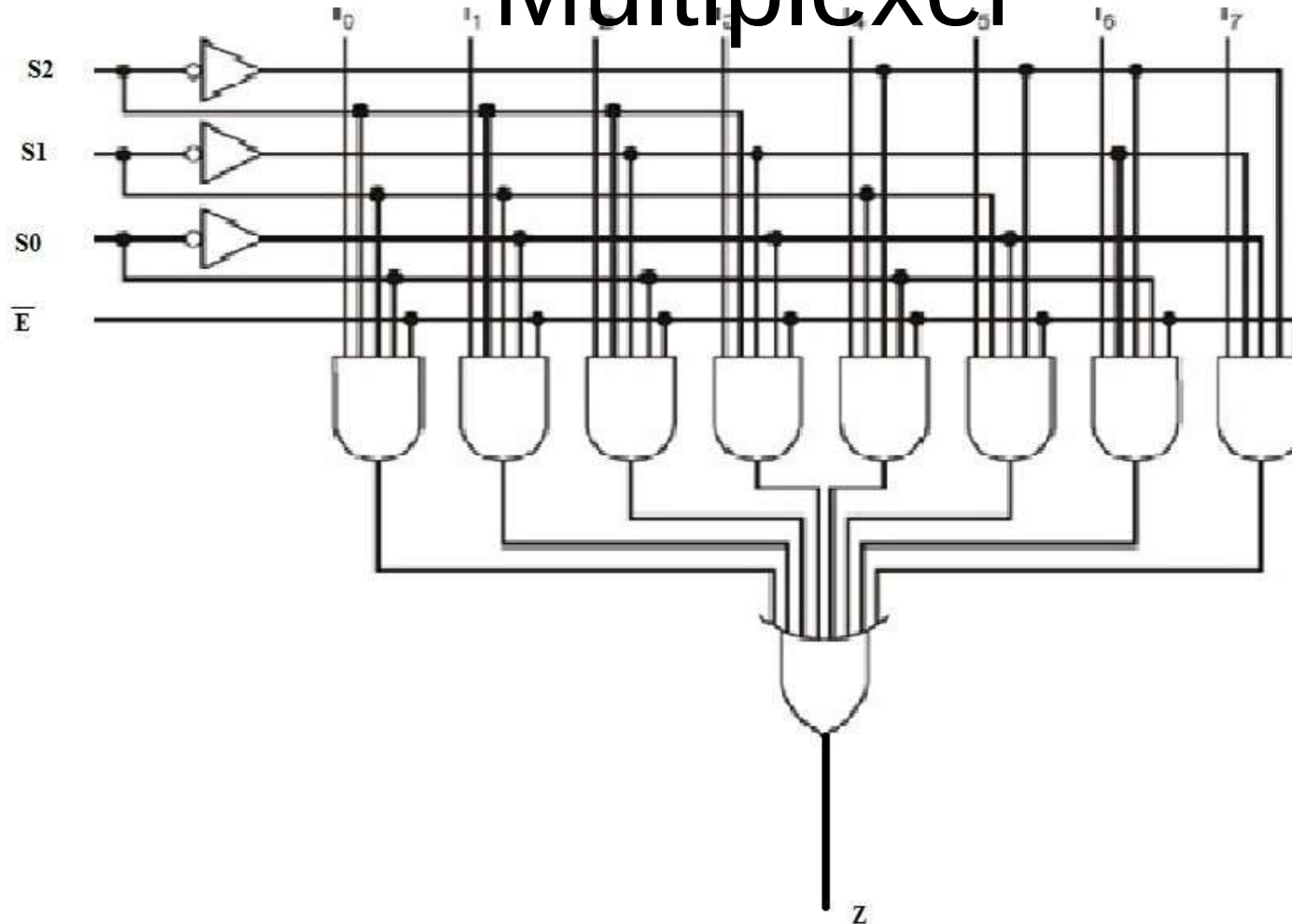


S_0	S_1	S_2	Z
0	0	0	I_0
0	0	1	I_1
0	1	0	I_2
0	1	1	I_3
1	0	0	I_4
1	0	1	I_5
1	1	0	I_6
1	1	1	I_7

Multiplexer TREE

- The Multiplexers with more number of inputs can be obtained by cascading two or more multiplexers with less number of inputs.

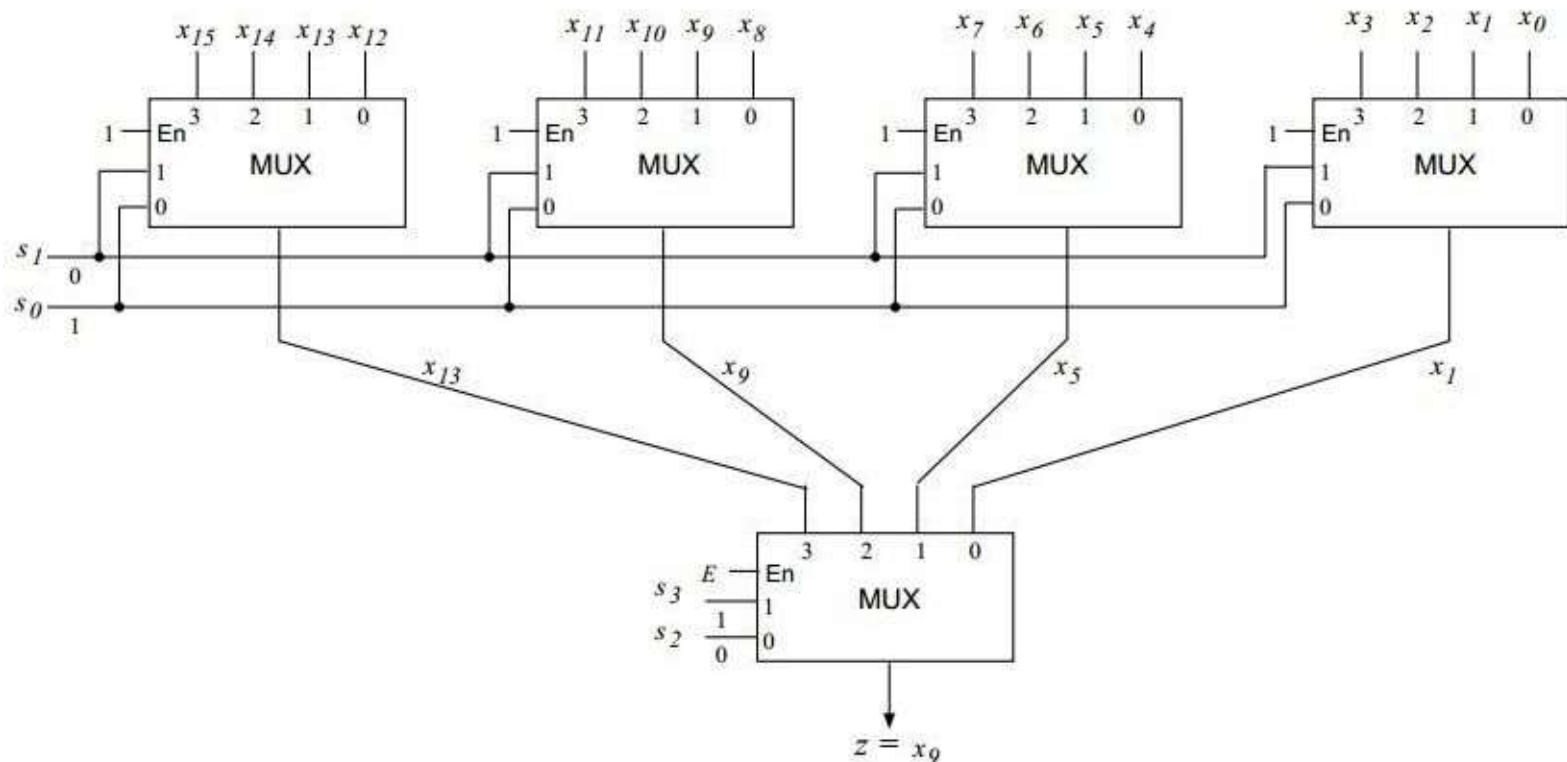Below is a design of 16:1 MUX using 4 4:1 MUXs :-




Demultiplexer (Data Distributor)

- Definition : A DEMULTIPLEXER (DEMUX) basically reverses the multiplexing function. It takes data from one line and distributes them to as given number of multiplexers. For this known as a data distributor.
- Single data input lines
- Some select line (less than the no. of output lines) Several output line
- If there are n data output lines and m select lines, then


$$2^m = n$$

Functional Diagram Of a Demultiplexer

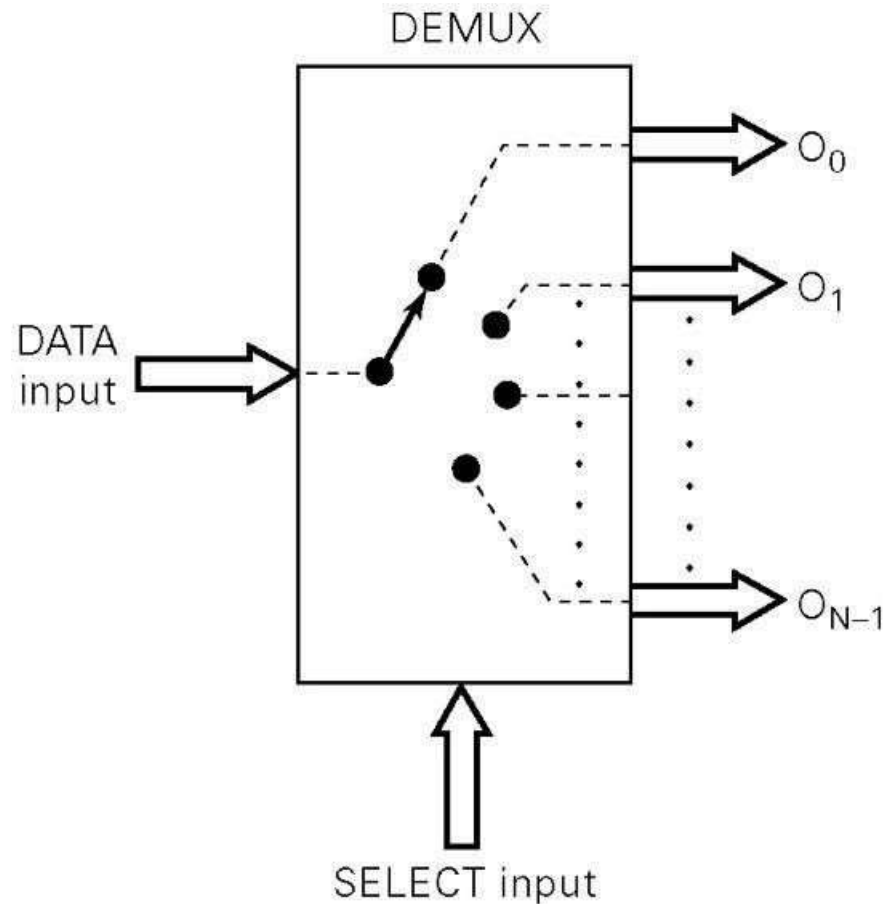


1 : 2

Demultiplexer

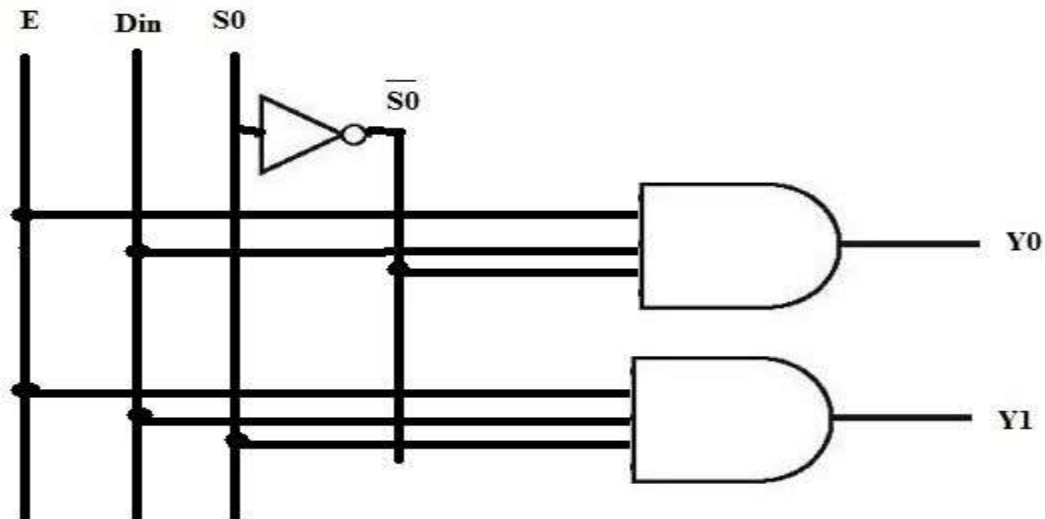

S_0	Y_0	Y_1
1	D	0
2	0	D


1 : 4

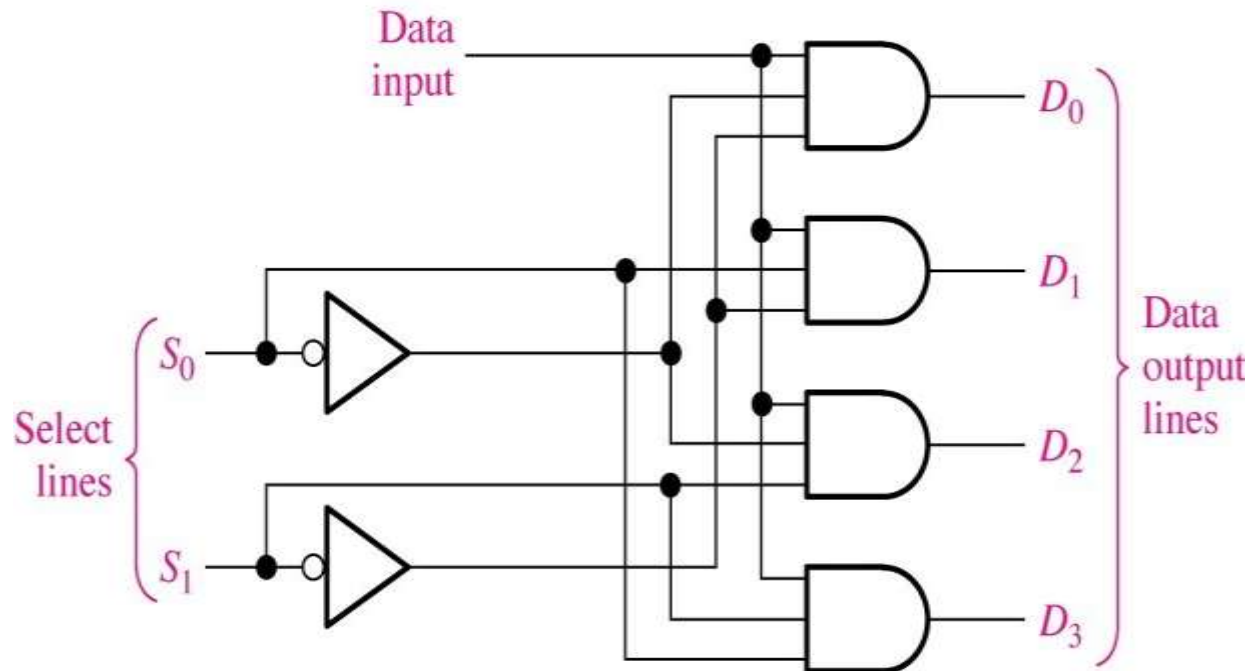

S_0	S_1	D_0	D_1	D_2	D_3
0	0	D	0	0	0
0	1	0	D	0	0
1	0	0	0	D	0
1	1	0	0	0	D

1 : 8

Demultiplexer

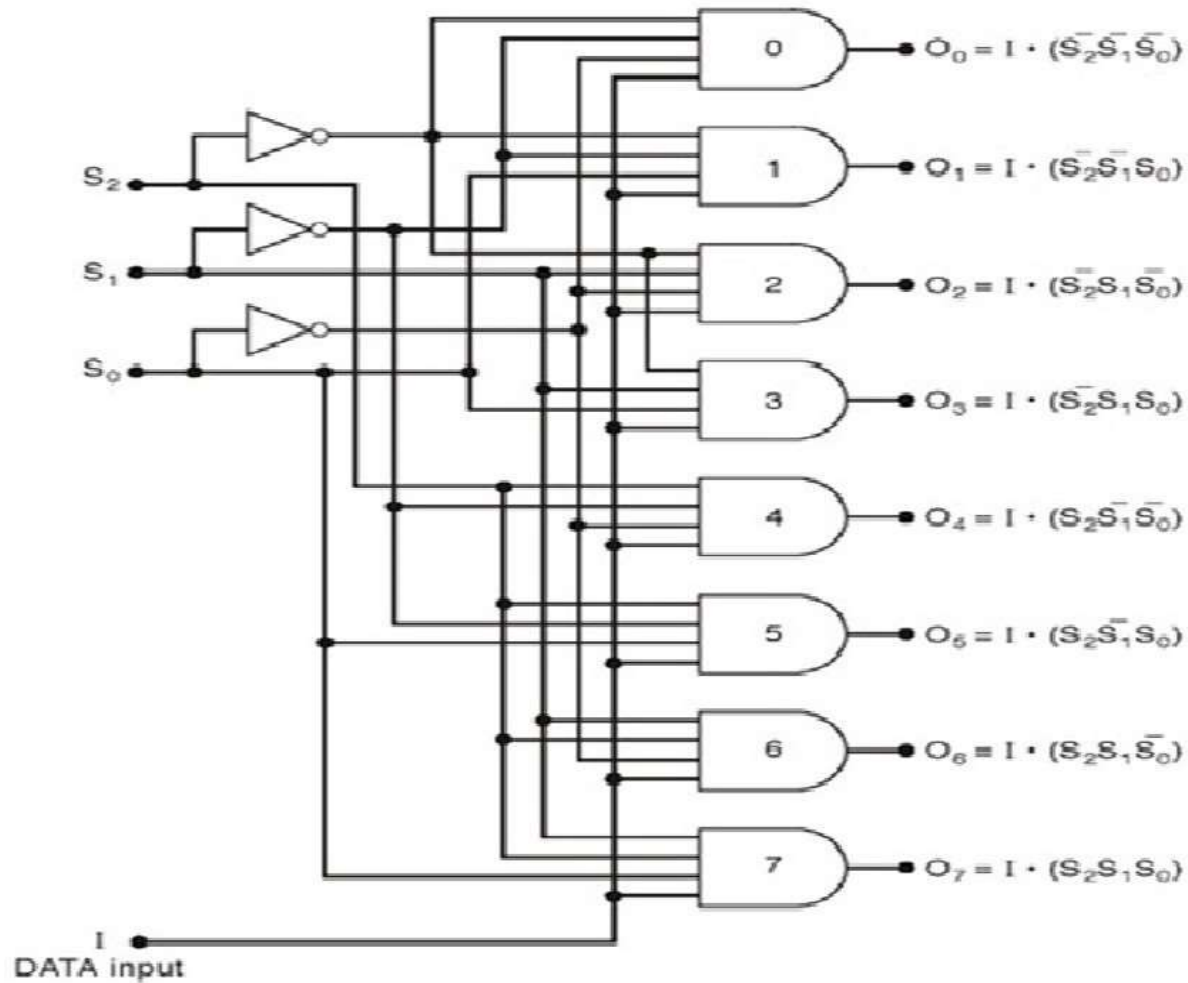

1 : 8 Demultiplexer (Truth Table)


S_0	S_1	S_3	D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7
0	0	0	D	0	0	0	0	0	0	0
0	0	1	0	D	0	0	0	0	0	0
0	1	0	0	0	D	0	0	0	0	0
0	1	1	0	0	0	D	0	0	0	0
1	0	0	0	0	0	0	D	0	0	0
1	0	1	0	0	0	0	0	D	0	0
1	1	0	0	0	0	0	0	0	D	0
1	1	1	0	0	0	0	0	0	0	D

Implementation Of Logic

Functions using Multiplexer


$$f(a, b, c) = a'b'c + ab$$

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

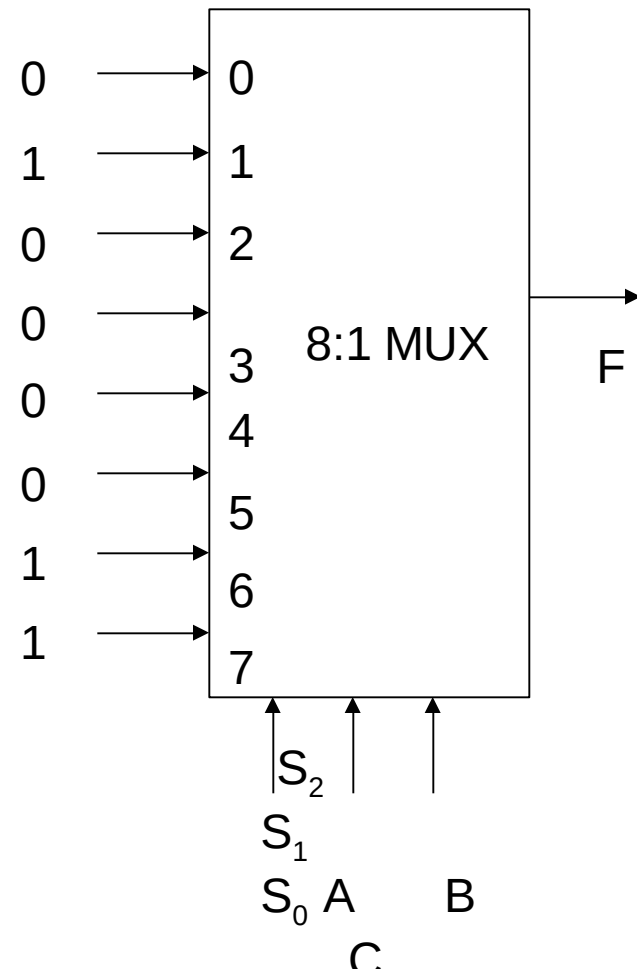

$$f(a, b, c) = a'b'c + ab$$

A	B	C	O	F
0	0	0	0	C
0	0	1	1	
0	1	0	0	0
0	1	1	0	
1	0	0	0	0
1	0	1	0	
1	1	0	1	1
1	1	1	1	

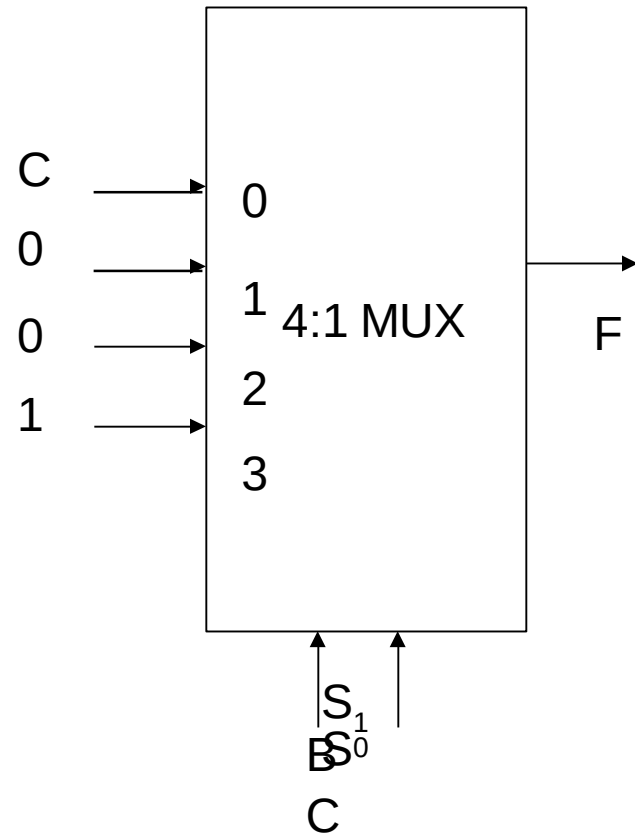

THANK
YOU