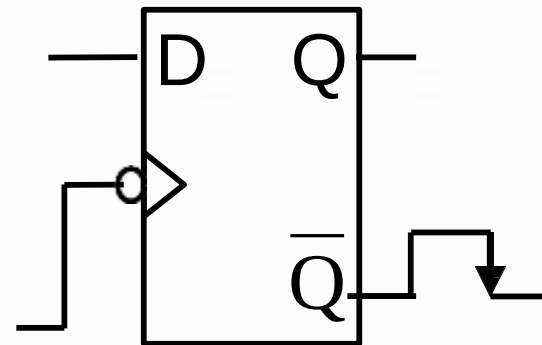


REGISTER



Introduction – Shift Register

- ◆ Shift registers are constructed using several flip-flop, connected in such a way to **STORE** and **TRANSFER/ Shift** digital data.
- ◆ Basically, D flip-flop is used. The input data (either '0' or '1') is applied to the D terminal and the data will be stored at Q during positive/negative-edge transition of the clock pulse.



Shift

Register

One D FF is used to store 1-bit of data. Thus, the number of flip-flops used is the same with the number of bit stored.

- Shift register mean that the data in each FF can be transferred/move to other FF upon edge triggering of the clock signal.
- Four types of data movement in shift register are:-
 - Serial in –serial out
 - Serial in – parallel out
 - Parallel in serial out
 - Parallel in – parallel out


Shift Register

Serial Data Vs Parallel Data movement

Serial	Parallel
• Movement of N-bit data require N number of CLK pulses. Thus, the operation is slow. • Only one FF is required to be connected at the output terminal, thus only one wire is required.	• Require only one CLK pulse to transfer all N-bit of data. Thus, operation is faster than serial. • Required N number of connection to the output terminal, which is proportional to the number of bit. Thus, too many connection is required.


Parallel in / parallel out (PIPO)

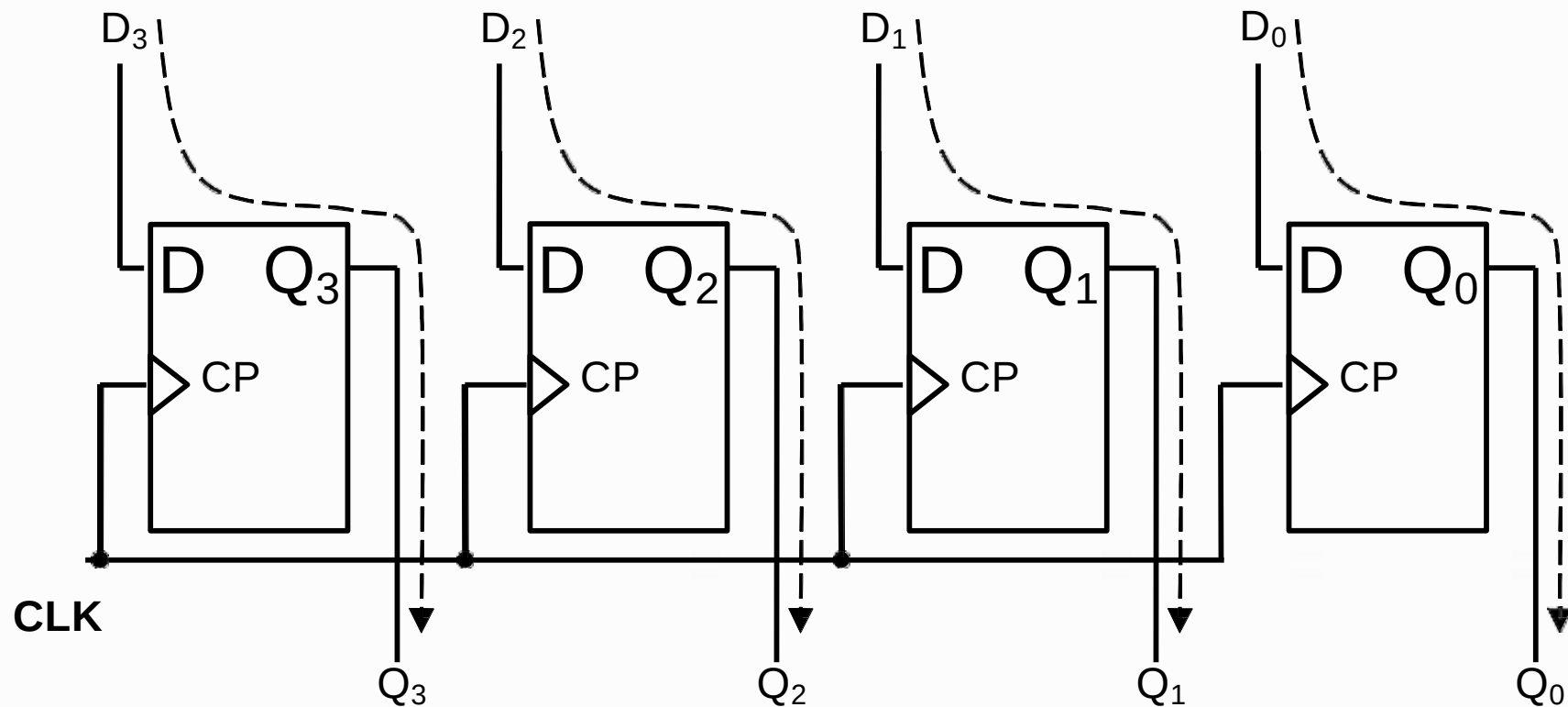◆ Flip-flop configuration for PIPO register.




Parallel in –parallel out (PIPO)

PIPO data movement.

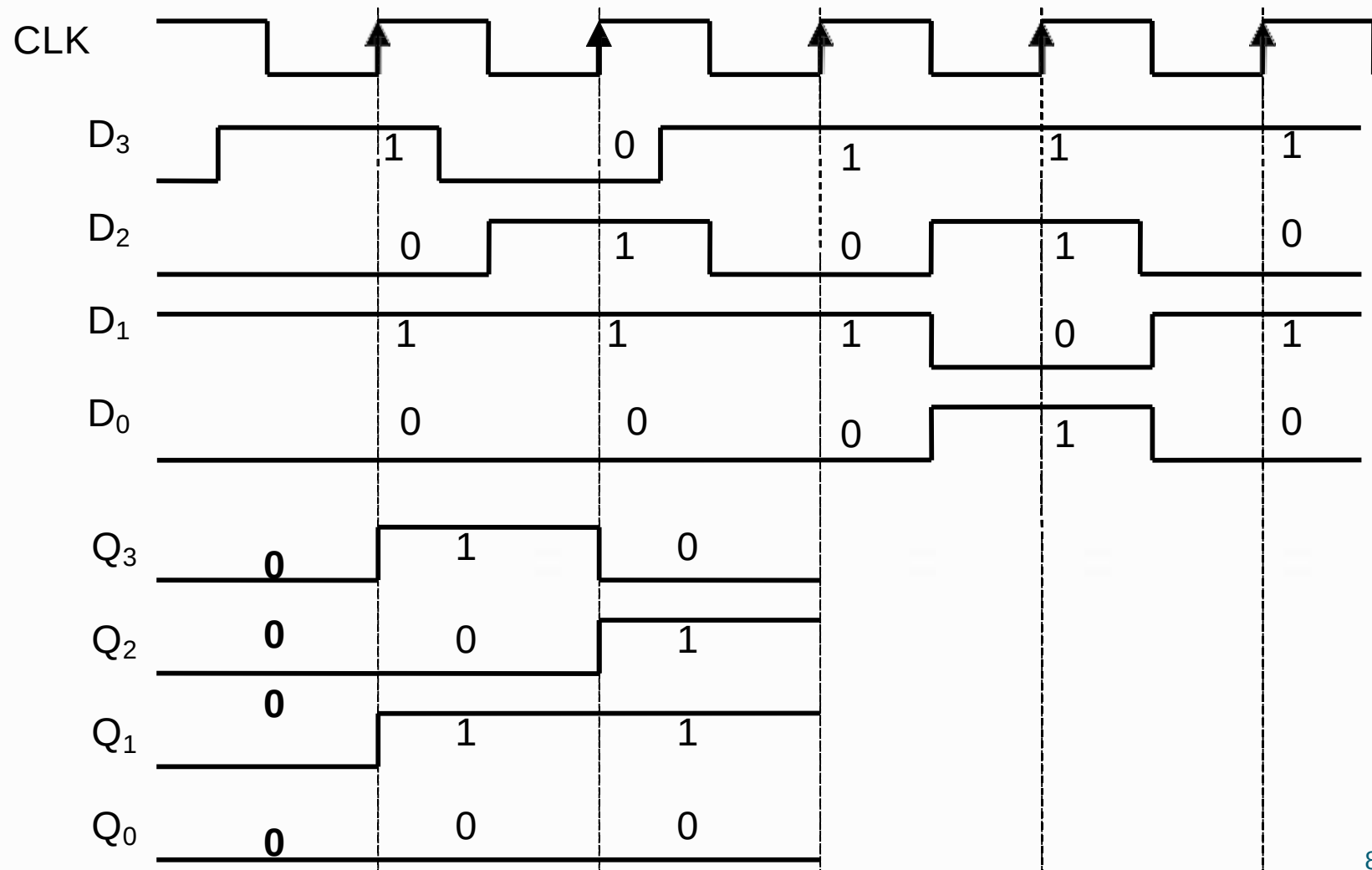


Serial in / serial out (SISO)

◆ Flip-flop connection for SISO.

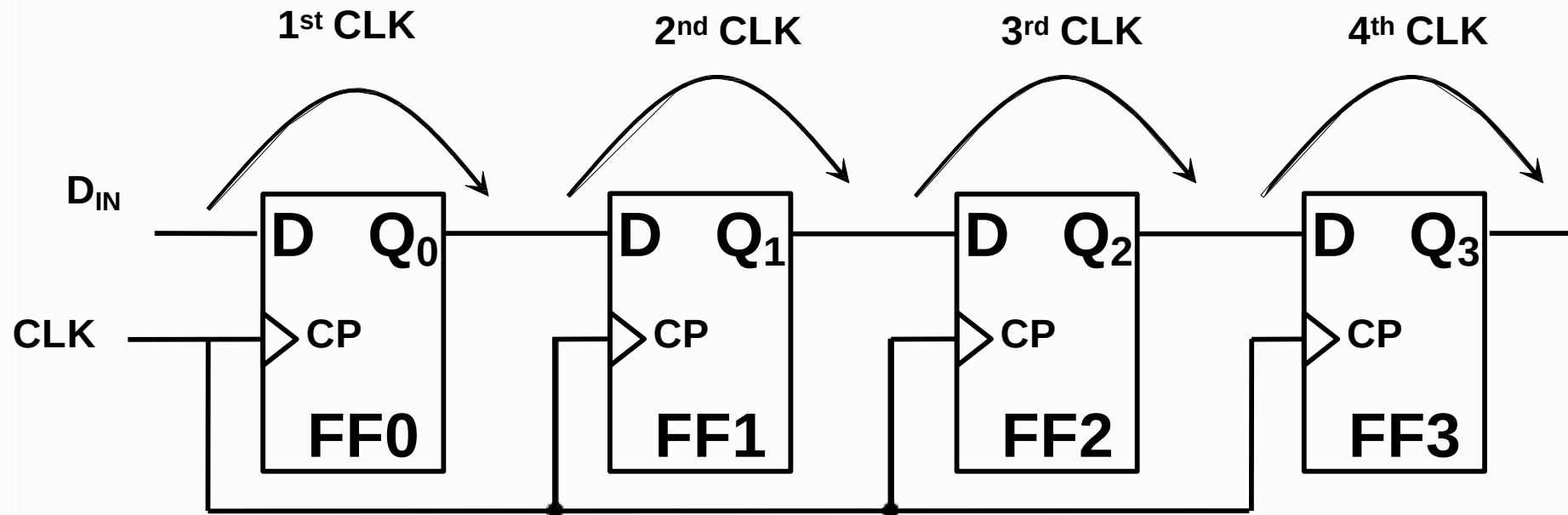


Serial in –serial out (SISO)

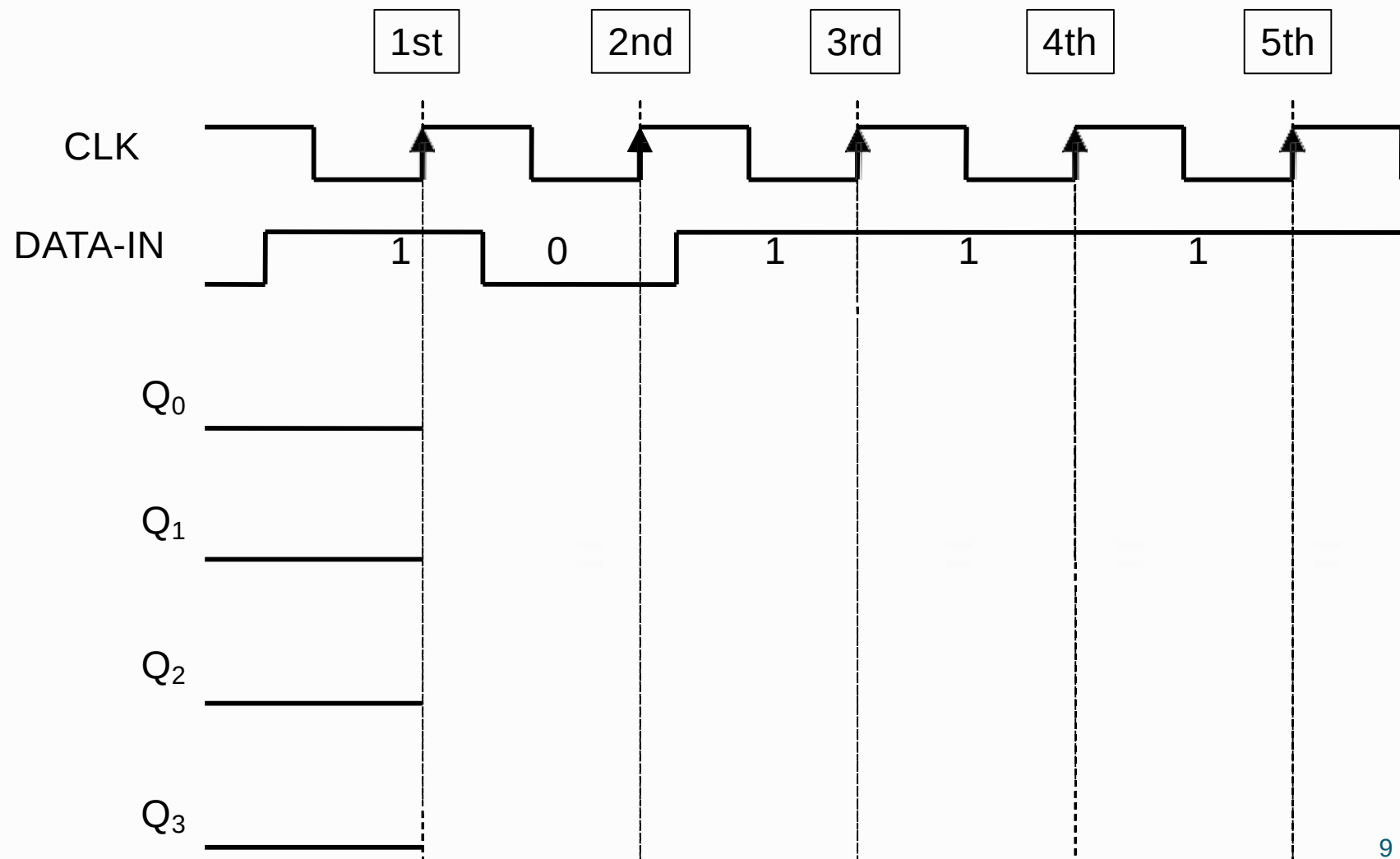SISO data movement. Binary data 10111 is transferred!




Parallel in / serial out (PISO)

Flip-flop connection for PISO

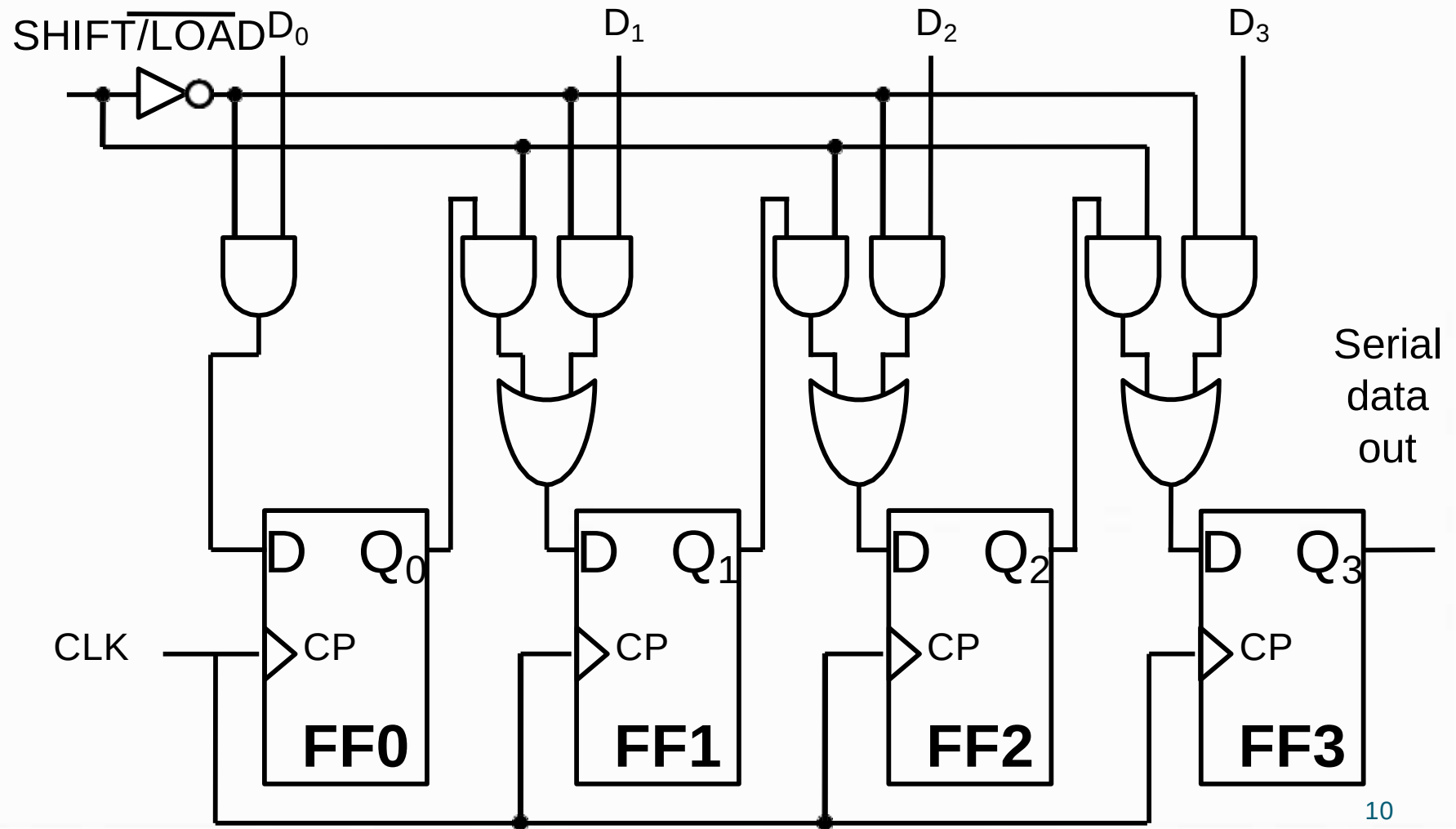


Part 1 (FFFBSSSS0000)

◆ PISO data movement.

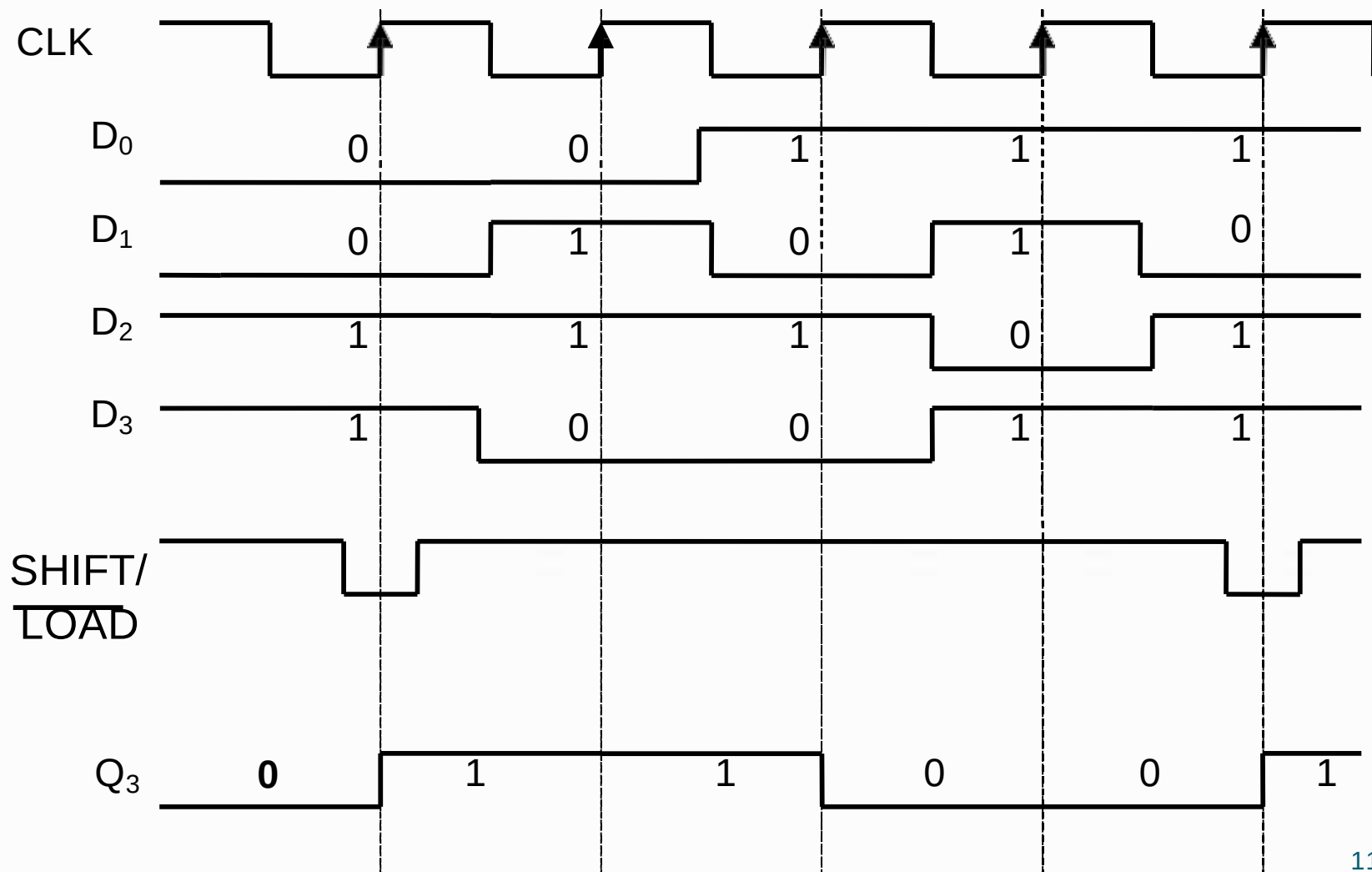


Chips for shift

74164 is a 8-bit SIPO shift register

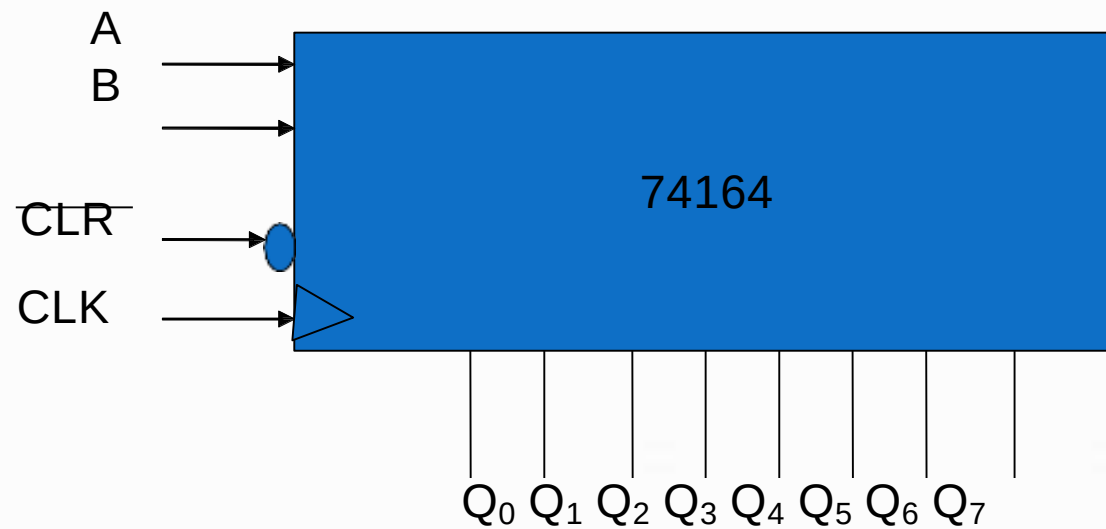


Chips for shift registers

❖ 74165 is a 8-bit PISO register

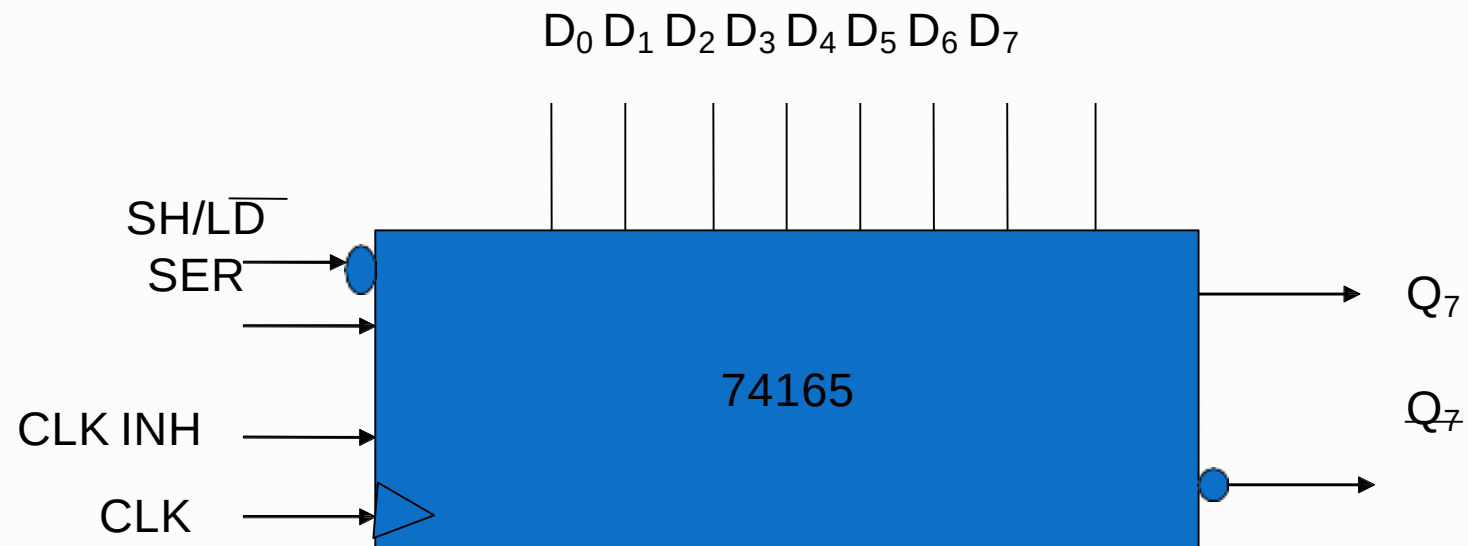


Chips for shift registers

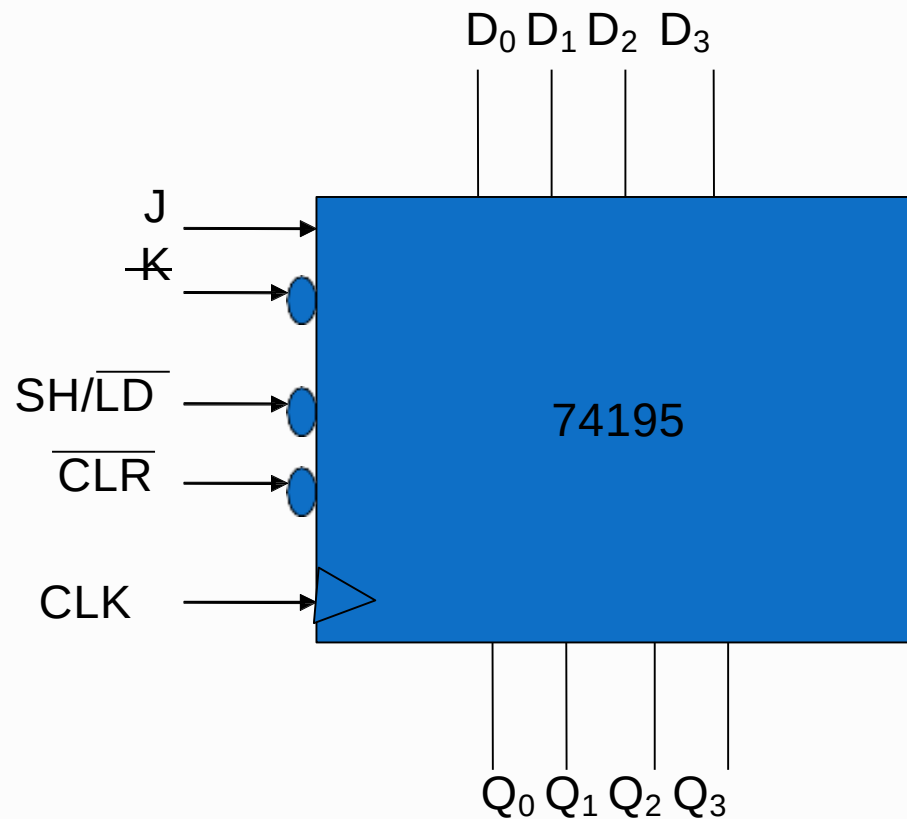
74195 can be used as a 4-bit PIPO register



Bidirectional shift register

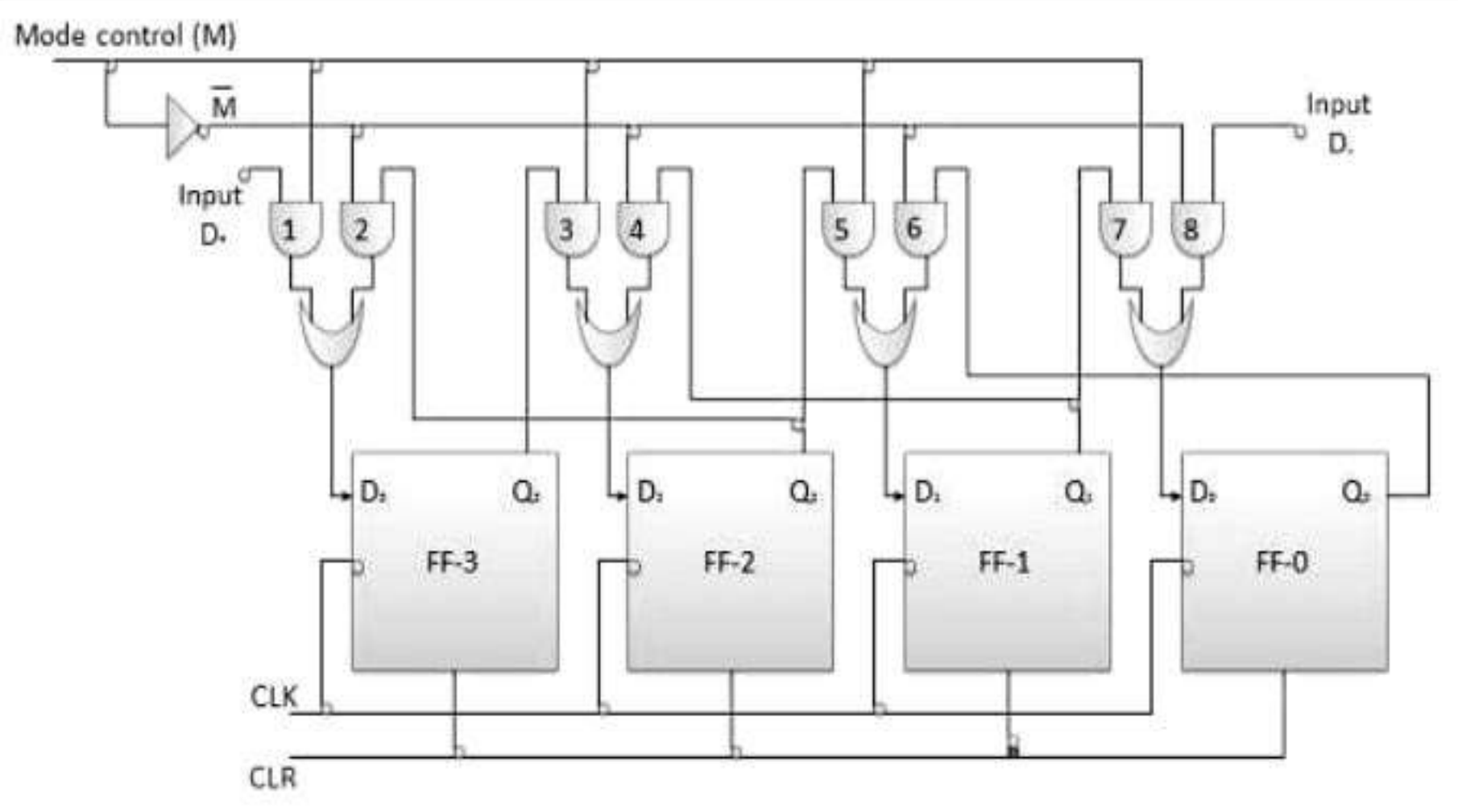

Universal shift register

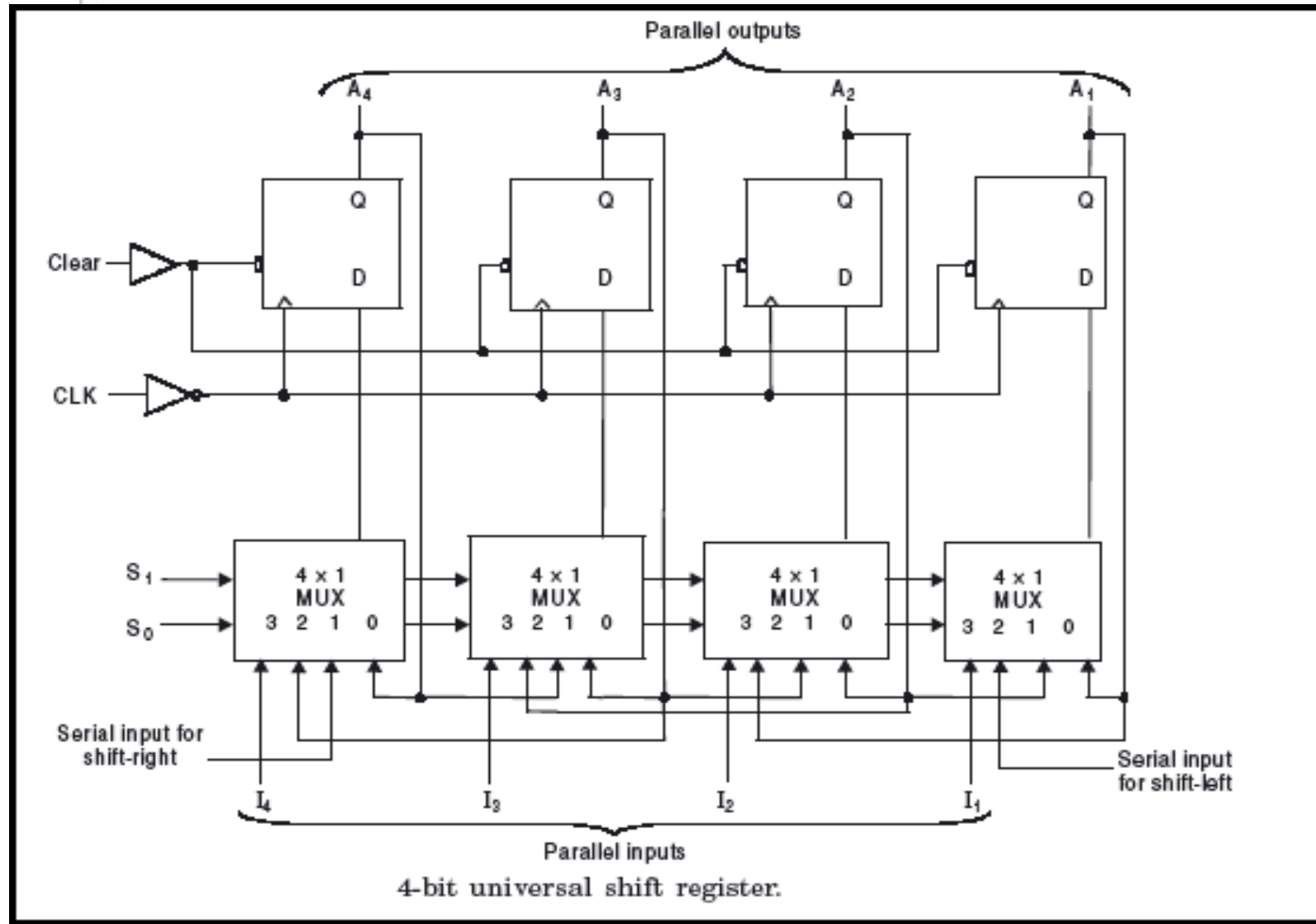

Shift Register Counters

◆ A whose output being fed back (connected back) to the serial input. This shift register would count the

state in a unique sequence!

◆ Two types of shift register counter:-

◆ ~~The ring counter~~


◆ ~~The Johnson counter~~

Ring Counter (continue)

- ❖ Ring counters are used to construct “One-Hot” counters
- ❖ It can be constructed for any desired MOD number
- ❖ A MOD-N ring counter uses N flip-flops connected in the arrangement as shown in fig.


a)

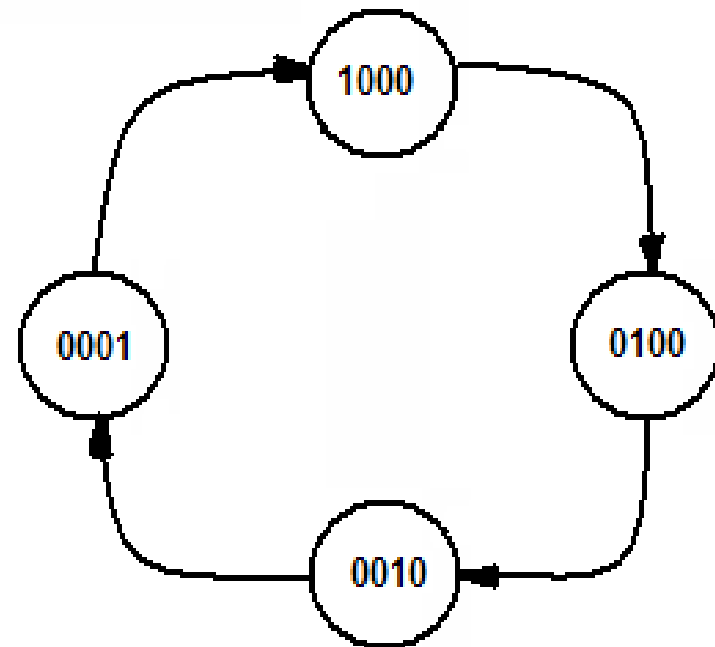- ❖ In general ring-counter will require more flip-flops than a binary counter for the same MOD number



d) State Diagram

Ring Counter

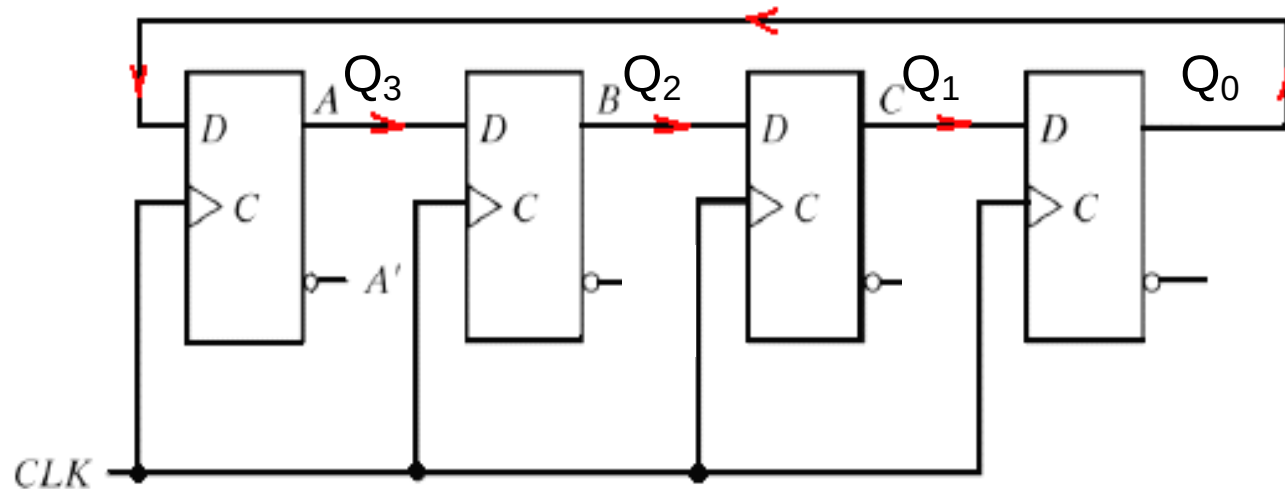


a) Four-bit ring counter

Ring Counter (continue)

Sequence Number	Flip-Flop outputs			
	A	B	C	E
1	1	0	0	0
2	0	1	0	0
3	0	0	1	0
4	0	0	0	1
5	1	0	0	0
6	0	1	0	0
7	0	0	1	0
8	0	0	0	1

c) Sequence table

Ring Counter (continue)

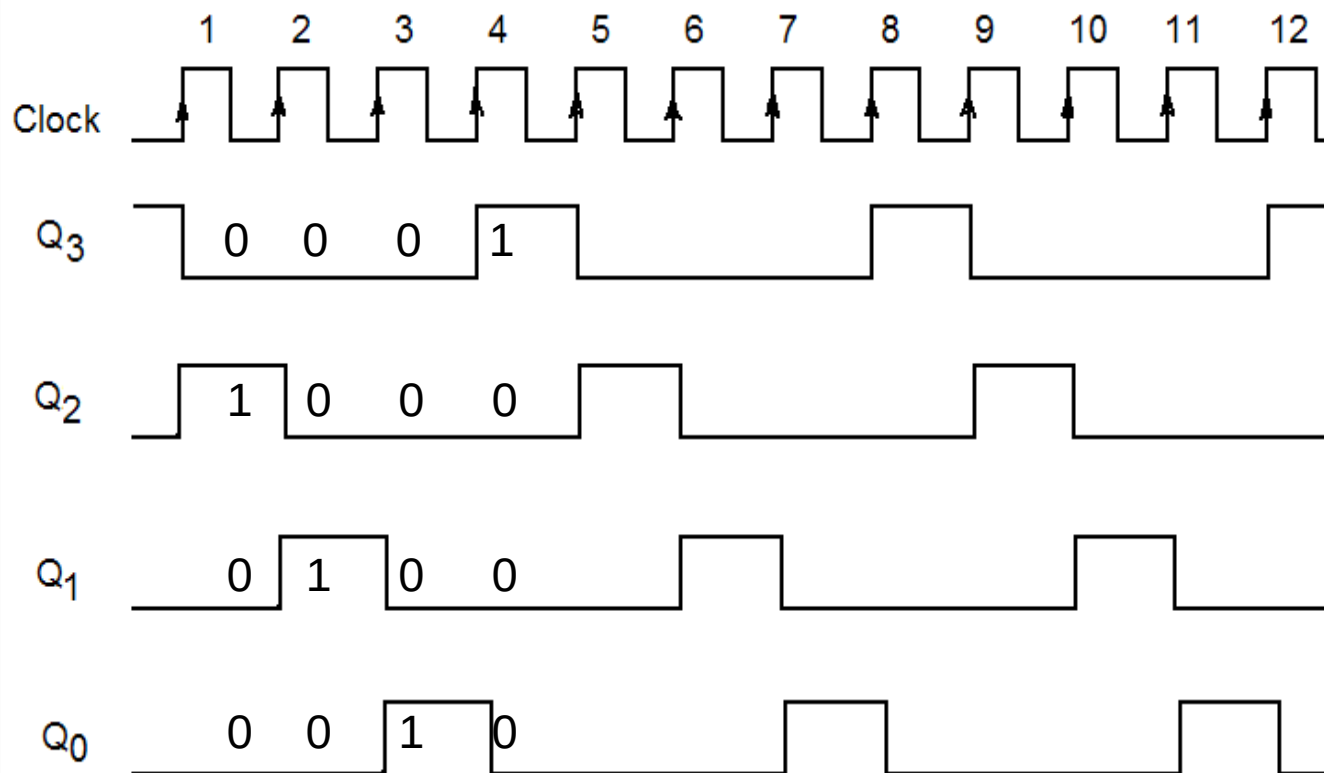

b) Four-bit ring counter waveform

Ring Counter (continue)


❖ Exercise: Draw a 3 Bit Ring Counter Circuit with initial input **010** . show a True Table until 8 clock pulse/number sequence and draw the output waveform.

❖ Answer:

Discuss with Your lecturer

Johnson Counter

Or Twisted-ring counter

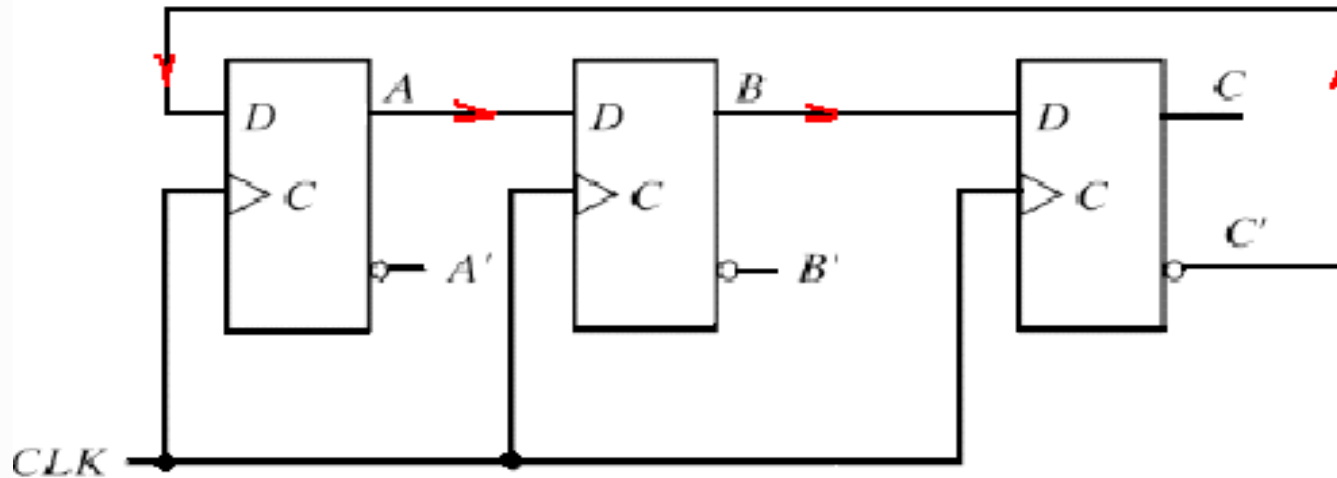


a) MOD-6 Johnson counter

- ◆ Johnson counter constructed exactly like a normal ring counter except that the inverted output of the last flip-flop is fed back to first flip-flop

Johnson Counter (Continue)


Sequence Number	Flip-Flop outputs		
	A	B	C
0	0	0	0
1	1	0	0
2	1	1	0
3	1	1	1
4	0	1	1
5	0	0	1
6	0	0	0
7	1	0	0
8	1	1	0
▪	▪	▪	▪
▪	▪	▪	▪
▪	▪	▪	▪

c) Johnson Counter sequence table

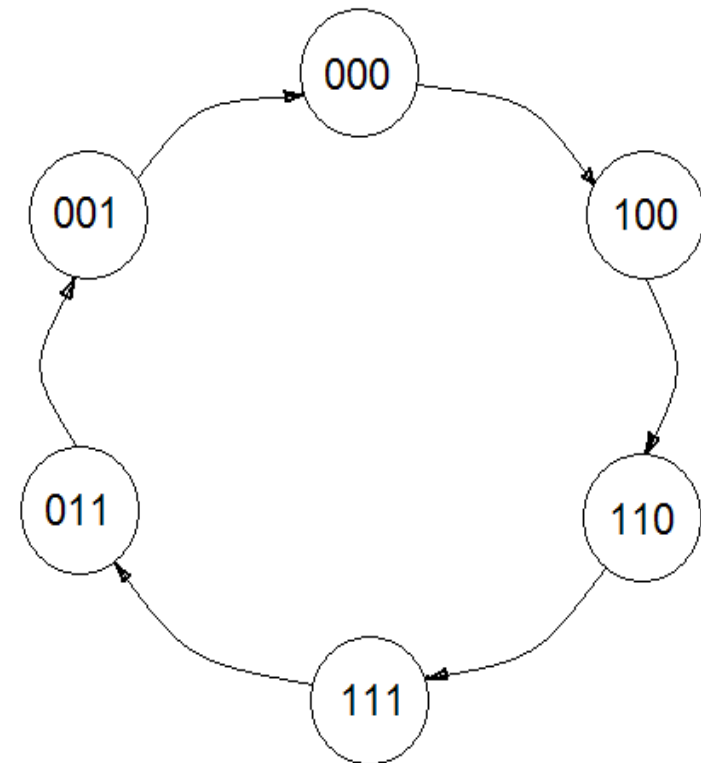

d) Johnson counter state diagram

Johnson Counter (Continue)

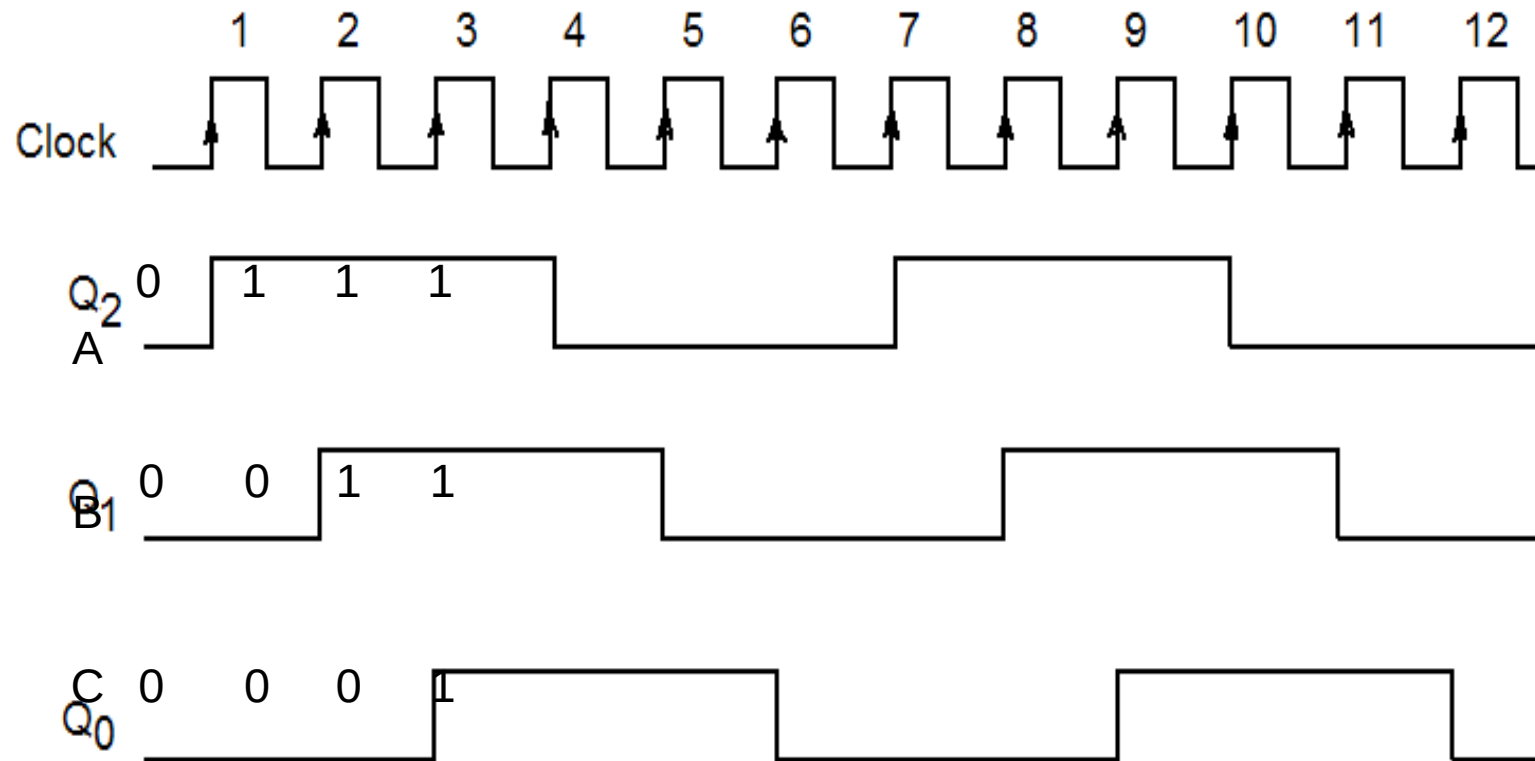

b) MOD-6 Johnson counter waveform


REFERENCES:

1. "Digital Systems Principles And Application"
Sixth Editon, Ronald J. Tocci.
2. "Digital Systems Fundamentals"
P.W Chandana Prasad, Lau Siong Hoe,
Dr. Ashutosh Kumar Singh, Muhammad Suryanata.


**Download Tutorials Chapter 6: Register
@ CIDOS**

<http://www.cidos.edu.my>

<http://www.sabariahsalihin.com>

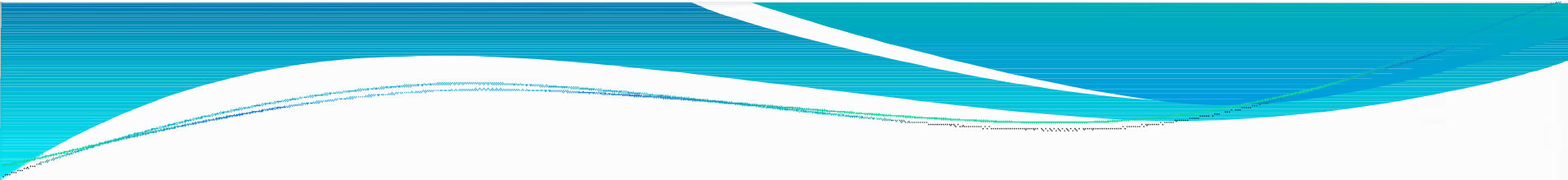

End Of This Topic

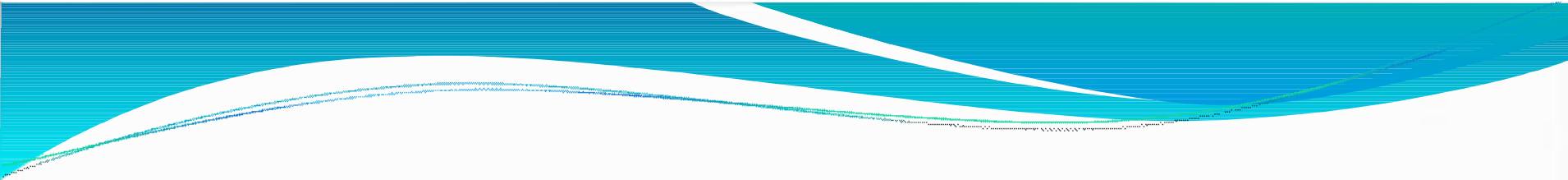

End Of This Topic