

ANALOG ELECTRONICS (3ETRC4)
B.E. 2nd YEAR ELECTRONICS & TELECOMMUNICATIONS

TEST #01

Max marks 20: Attempt all questions . Do not use unfair means . Each question is of 05 Marks.
Supplementary copies not allowed.

1. Draw input and output characteristic of common base configuration using PNP transistor. Your diagrams must be well labelled with dummy values of current and voltages.
2. If you are given input and output characteristics of common emitter amplifier ,also Q point is mentioned on it. Explain ,how will you calculate h_{oe} parameter from these graphs .
3. Convert h_{re} in terms of common base parameters.
4. For the composite transistor shown in figure , calculate h'_{ib} parameter of modified transistor using original common base H parameters considering R_b as part of modified transistor.

