

3EIRC2: Digital Electronics

II Year Electronics & Instrumentation Engg.

Time: 70 Minutes

Maximum Marks: 20

- Q1. What is meant by modulus of counter? Draw circuit for 4 bit Synchronous down counter Using J-K F/F. Explain working with excitation table and the count-table. 7
- Q2. Describe the principle of Binary Weighted Resistive ladder network for Digital to Analog conversion. 4
- Q3. Describe Dual slope integration technique using block diagram for Analog to Digital conversion. 4
- Q4. Draw Full Adder circuit and its truth-table. Write VHDL code for the same with Data flow architecture. 5